

For more
info:

www.MrCircuitTechnology.com

Gary@MrCircuitTechnology.com

Mr Circuit Technology

Science/Electronics Experiment Kits and Labs


“HOW A PHOTOCELL WORKS”

LESSON PLAN

Table of Contents

Page 01 - Explanation of the Experiment
 Page 02 - Purpose of the Experiment and Parts Needed
 Page 03 - Do the Experiment (part 1 of 2)
 Page 04 - Do the Experiment (part 2 of 2)
 Page 05 - Crossword Puzzle
 Page 06 - Word Search Puzzle
 Page 07 - Written 10-Question Multiple Choice Quiz
 Page 08 - Answers to Crossword
 Page 09 - Answers to Word Search
 Page 10 - Answer Key to Written Quiz
 Page 11 - Poster to put up on classroom wall
 Page 12 - Price List for Parts Kits for your to order more. Send
 Purchase Order to Gary@MrCircuitTechnology.com or
 order online at www.MrCircuitTechnology.com

Experiment Parts Kit
#MC1-00-PK
 Solderless
 Circuit Board
 Exciting, Educational
 and Fun



Experiment Parts only
 (packaged in a 3x5 inch
 resealable plastic bag.)

**LEARN more today,
 EARN more tomorrow!**


Copyright © Mr Circuit Technology 2024

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com

Science/Electronics Kits and Labs

Mr Circuit Technology

Experiment Parts Kit
#MC1-03-PK
 “How a Photocell
 Works”
 Exciting, Educational
 and Fun



Experiment Parts only
 (packaged in a 3x5 inch
 resealable plastic bag.)



**LEARN more today,
 EARN more tomorrow!**

Copyright © Mr Circuit Technology 2024

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com

Science/Electronics Kits and Labs

Mr Circuit Technology

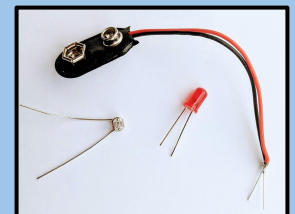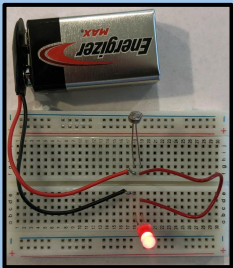

PREPARATION: You can put the Page 11 poster up on your classroom wall to announce the fact that you are going to do the Science-Electronics Experiment.

Step 1 - Make a copy of pages 1 through 7 for each student. The students can read and do these pages on their own or you can guide them.

Step 2 - Hand out Parts Kit #MC1-00-PK (that has the Solderless Circuit Board) and Parts Kit #MC1-03-PK (that has the experiment parts) with a 9-Volt battery. Give these items to each student along with the 7 pages.

Step 3 - When your students have completed the experiment, collect all the Parts Kits and batteries for later use.


Step 4 - Collect all the Written Quizzes for grading and use the Answer Key to grade them.

For Tech Support or any questions, you can email us or call 805-295-1642

EXPLANATION OF EXPERIMENT

*** You are going to build a circuit to observe a PHOTOCELL varying the current flow in a circuit.

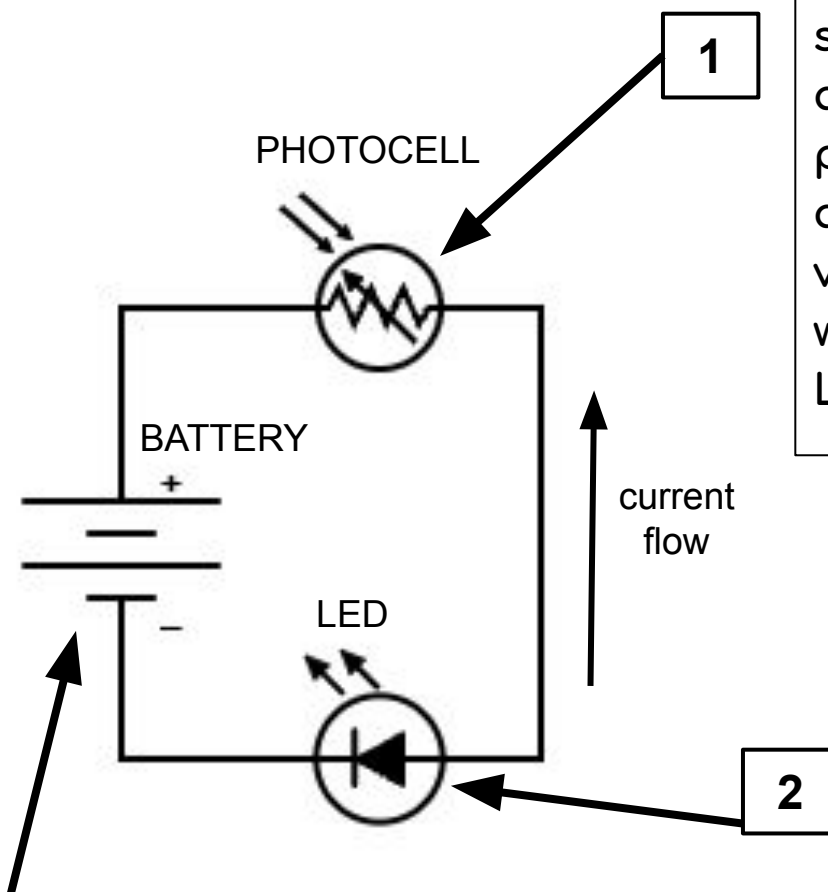Here is the SCHEMATIC DIAGRAM of the circuit you will build.



This circle with a squiggly line inside and two arrows pointing in represents a PHOTOCELL which varies its resistance with light. MORE light, LESS resistance.

The LED symbol (a circle with an arrow in it) represents a light-emitting diode that lights up when electric current is flowing through it.

The symbol (with the straight lines and a plus and minus sign) represents a BATTERY.

The electron current in this circuit flows out of the negative side of the battery through the LED, through the PHOTOCELL and then back to the positive side of the battery.

(Continue to Page 2)

PURPOSE OF THIS EXPERIMENT

*** To observe a PHOTOCELL varying current flow in a circuit.

PARTS NEEDED FOR EXPERIMENT

In this experiment, you will use a BATTERY SNAP


a PHOTOCELL



an LED



and a SOLDERLESS CIRCUIT BOARD.

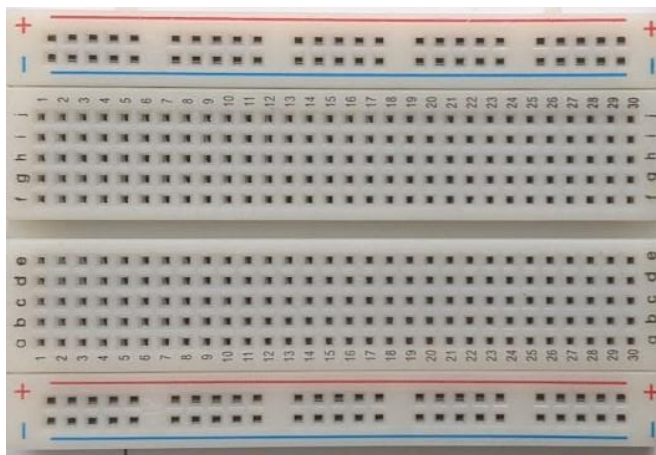


You will also need a good 9 Volt battery
(Continue to Page 3)

DO THE EXPERIMENT (part 1 of 2)

MC1-03-R-3

*** You are going to build a circuit to demonstrate how a PHOTOCELL varies the amount of current in a circuit.

Step 1 - Take out a Battery Snap and install it with its Red lead in hole 18f and its Black lead in hole 18e as shown in the pictorial diagram. (Note: If you reverse the leads, the circuit will NOT work.)

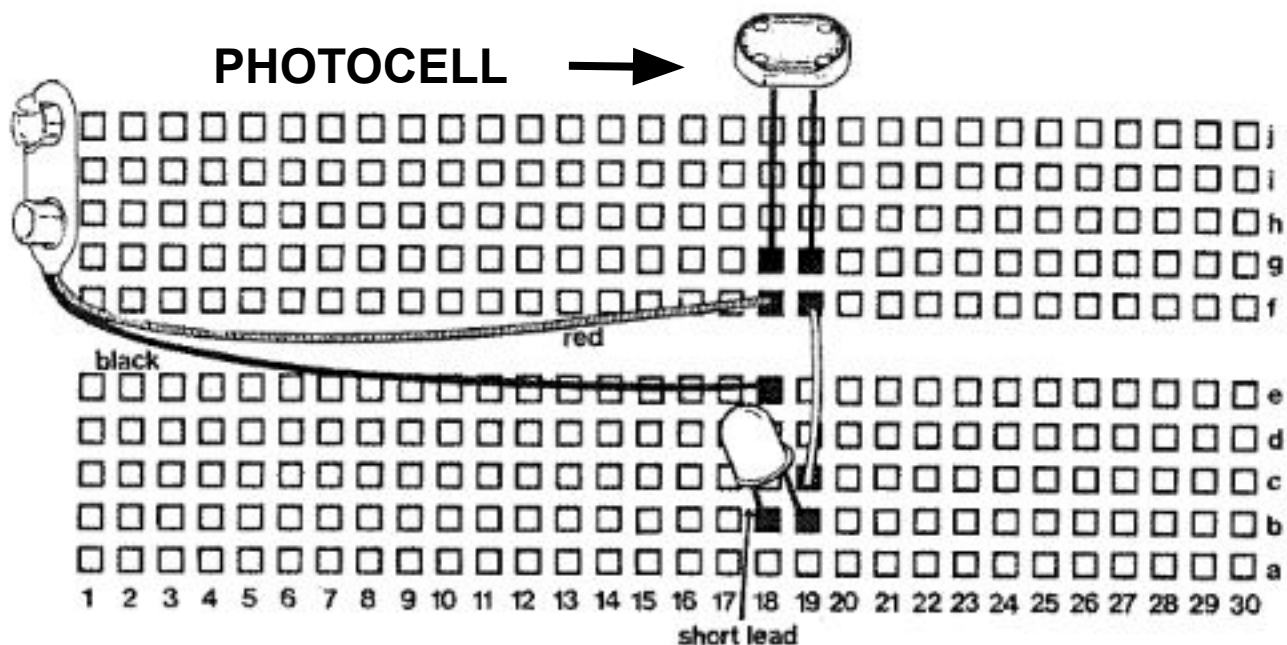PICTORIAL DIAGRAM

Step 2 - Install an LED with its short lead into hole 18b and its long lead into hole 19b.


Step 3 - Install the PHOTOCELL as shown on the pictorial into holes 18g and 19g. (Note: A PHOTOCELL does not have polarity so there is no positive or negative side.)

(Continue to Page 4)

DO THE EXPERIMENT (part 2 of 2)

MC1-03-R-4


Step 5 - Connect the battery to the battery snap and observe how the LED lights up. Then put your finger on top of the LED. How does that affect the brightness of the LED.

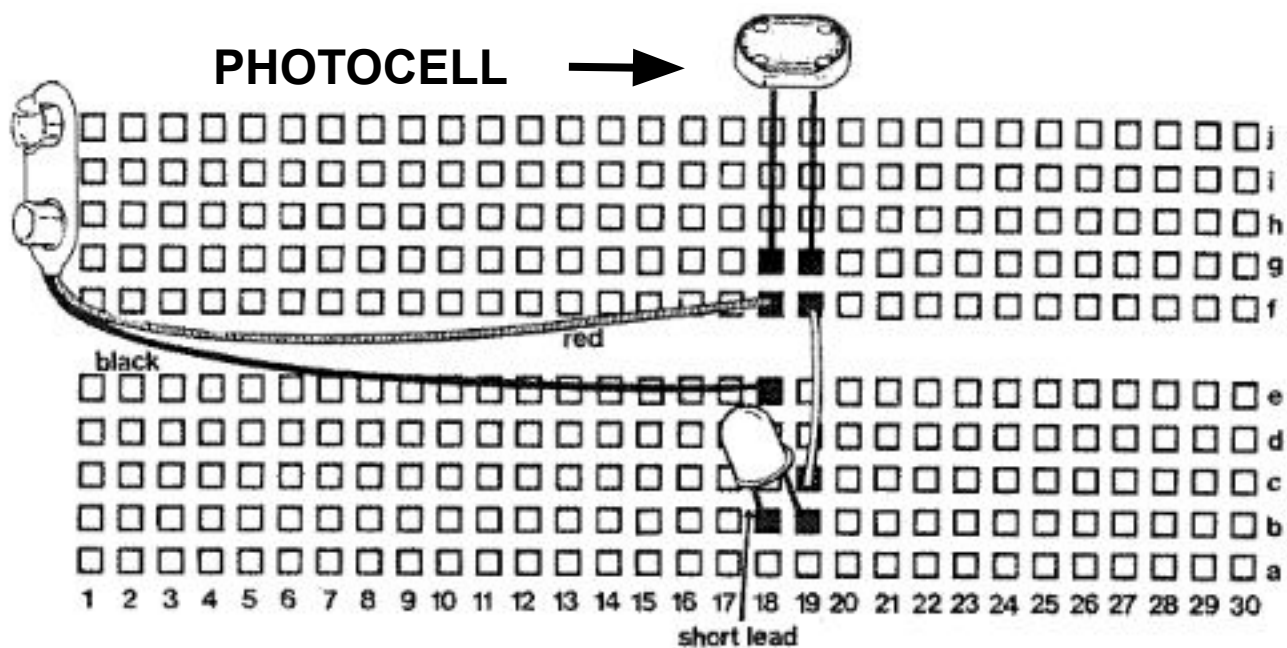PICTORIAL DIAGRAM**CONCLUSION**

*** You should have noticed that when you cover the light from hitting the PHOTOCELL, the LED gets dimmer. So, a PHOTOCELL increases its resistance when the light is diminished. The MORE light hitting the PHOTOCELL, the LESS resistance. So, the MORE light hitting the PHOTOCELL, the brighter the LED.

(End of Experiment 3)

Experiment 3 - "How A PHOTOCELL Works"

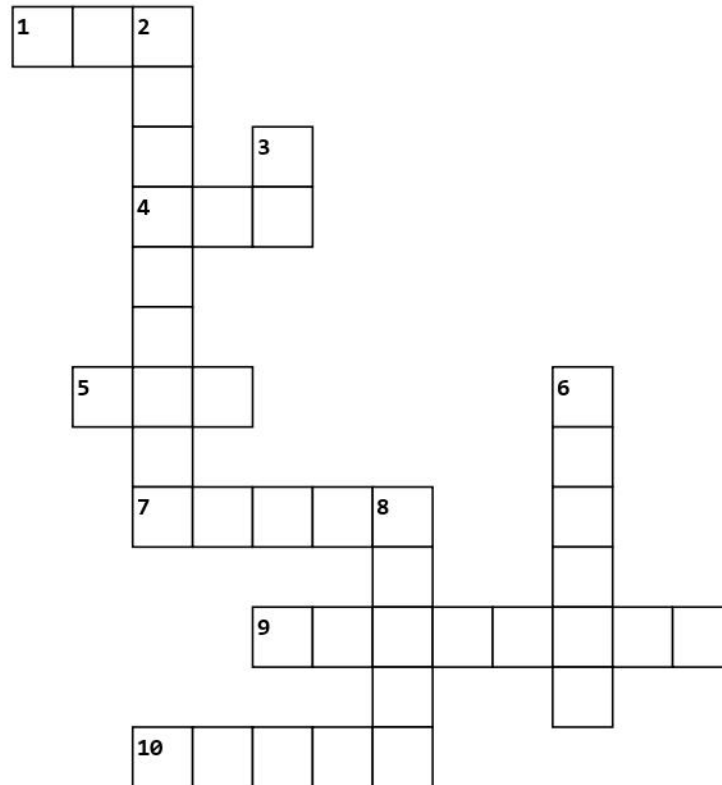

Across

1. What part of the PHOTOCELL is sensitive to light?
4. How many leads does a PHOTOCELL have?
5. Does an LED have polarity?
7. What causes the PHOTOCELL to vary its resistance?
9. What will cause the resistance of the PHOTOCELL to increase?
10. True or False, an LED is sensitive to light?

Down

2. This circuit has an LED, a _____, and a BATTERY.
3. Does a PHOTOCELL have polarity?
6. What do you use to shield the light from hitting the PHOTOCELL?
8. This circuit has how many electronic parts?

Experiment 3 - "How A PHOTOCELL Works"

Z S N L V M W F V N Y Y G A B Q V L U A
H Q E R J F K A N Y V N F T Y R A J R L
P Q Z E Z R H L Y O D T J N C Y Y O F S
G N K X S F V S X G G Z L L U L L R Z E
V I O T Q T Y E M E R Y B J K L G L M O
F F B N W W U B G W C E W L Y E O M X E
S B Q S Q O R H R O K S I O G C O D C X
A A D M E Y M B V E A P G X J O W J W G
P P L V D Z V N Q Q L I G H T T S M T S
U L S G V I N Q J M F K H T H O E E U X
U R S W K T S G P U T N E Q O H D E E E
C M S K K J U F M E Y K Y V T P X R R D
V O E P U D K W A N D X A L H I P H L P
Y C N X T G L Z J A K Q J H H D F T I O
S P K G D A U F J K R R A R C G Z Y C T
K M R V I Z X F W P C Q S C K I J P K I
V V A M H O L C Y E E H T J I C W M U S
O T D N D T O U I P K A L S T U U Y Z R
J Y K C H G F I N G E R V S J H B B F U
N L W O N X U K W O V Y N T Y B W W V X

1. How many leads does a PHOTOCELL have?
2. Does a PHOTOCELL have polarity?
3. What causes the PHOTOCELL to vary its resistance?
4. What part of the PHOTOCELL is sensitive to light?
5. Does an LED have polarity?
6. What will cause the resistance of the PHOTOCELL to increase?
7. This circuit has how many electronic parts?
8. What do you use to shield the light from hitting the PHOTOCELL?
9. This circuit has an LED, a _____, and a BATTERY.
10. True or False, an LED is sensitive to light?



QUIZ for Exp 03 or STEM KIT #03 in the Mr Circuit Electronics Training Lab 1

This Quiz covers the training learned by completing

“How a Photocell Works” Experiment 3



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

- A
B
C
D

#1 How many leads does a Photocell have?
A. 1
B. 2
C. 3
D. 6

#6 This circuit has three components. They are the battery snap, a resistor, and a _____.
A. Photocell
B. Potentiometer
C. capacitor
D. microphone

- A
B
C
D

- A
B
C
D

#2 Does a Photocell have polarity?
A. YES
B. NO
C. maybe
D. not necessarily

#7 In this experiment, what do we use to shield the light from hitting the Photocell?
A. a flashlight
B. a fork
C. a hand
D. a forklift

- A
B
C
D

- A
B
C
D

#3 In order for a Photocell to vary its resistance, light has to hit the _____.
A. top surface
B. bottom surface
C. the leads
D. the left side

#8 A Photocell changes its resistance because it is sensitive to _____.
A. air
B. pressure
C. gravity
D. light

- A
B
C
D

- A
B
C
D

#4 If you reverse the leads on the battery snap, how will that affect the circuit?
A. the LED will be brighter
B. the circuit will work just fine
C. the LED will get hot and burn up
D. the LED will not light up

#9 When you block the amount of light hitting a Photocell, its resistance _____.
A. is not affected
B. decreases
C. causes more capacitance in the circuit
D. increases

- A
B
C
D

- A
B
C
D

#5 If you put this circuit into a dark room, how will that affect the LED brightness?
A. it will be super bright
B. it will burn out
C. it will be dimmer
D. it will be the same as in bright light


#10 How does the brightness of the light that hits the Photocell affect the LED in the circuit?
A. has no effect at all
B. brighter the light, brighter the LED
C. LEDs don't get brighter or dimmer
D. dimmer the light, brighter the LED

- A
B
C
D

Score []

ANSWERS FOR CROSSWORD

Experiment 3 - "How A PHOTOCELL Works"

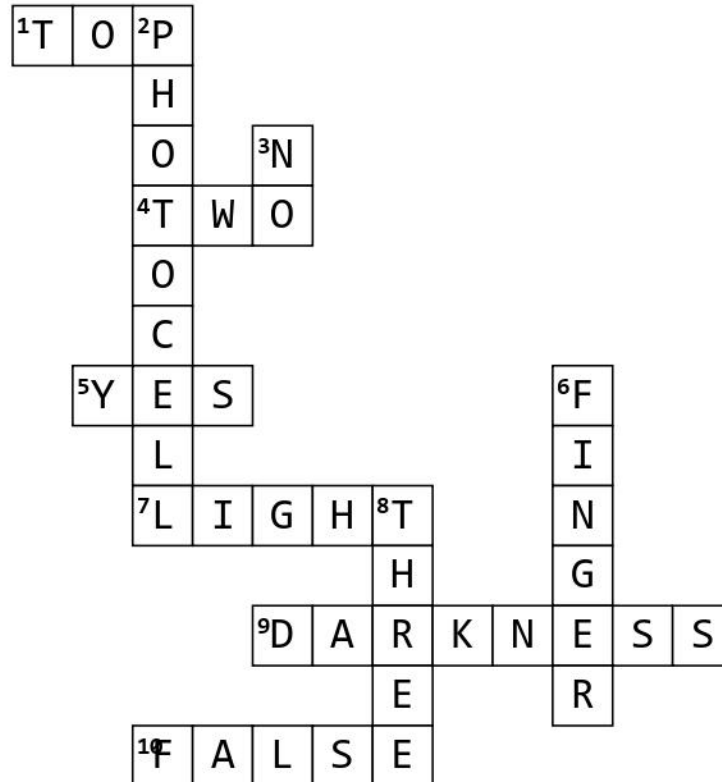

Across

1. What part of the PHOTOCELL is sensitive to light?
4. How many leads does a PHOTOCELL have?
5. Does an LED have polarity?
7. What causes the PHOTOCELL to vary its resistance?
9. What will cause the resistance of the PHOTOCELL to increase?
10. True or False, an LED is sensitive to light?

Down

2. This circuit has an LED, a _____, and a BATTERY.
3. Does a PHOTOCELL have polarity?
6. What do you use to shield the light from hitting the PHOTOCELL?
8. This circuit has how many electronic parts?

ANSWERS FOR WORD SEARCH

Experiment 3 - "How A PHOTOCELL Works"


Z S N L V M W **F** V N Y Y G A B Q V L U A
 H Q E R J F K **A** **N** Y V N F T Y R A J R L
 P Q Z E Z R H L **Y** O D T J N C Y Y O F S
 G N K X S F V **S** X G G Z L L U **L** L R Z E
 V I O T Q **T** Y **E** M E R **Y** B J K L G L M O
 F F B N W **W** U B G W C **E** W L Y E O M X E
 S B Q S Q **O** R H R O K **S** I O G C O D C X
 A A D M E Y M B V E A P G X J O W J W G
 P P L V D Z V N Q Q **L I G H T** T S M T S
 U L S G V I N Q J M F K H T H O E **E** U X
 U R **S** W K T S G P U T N E Q O H D E E E
 C M **S** K K J U F M E Y K Y V T **P** X R R D
 V O **E** P U D K W A N D X A L H I P H L **P**
 Y C N X T G L Z J A K Q J H H D F **T** I O
 S P K G D A U F J K R R A R C G Z Y C T
 K M R V I Z X F W P C Q S C K I J P K I
 V V A M H O L C Y E E H T J I C W M U S
 O T **D** N D T O U I P K A L S T U U Y Z R
 J Y K C H G **F I N G E R** V S J H B B F U
 N L W O N X U K W O V Y N T Y B W W V X

1. How many leads does a PHOTOCELL have? 2. Does a PHOTOCELL have polarity?
3. What causes the PHOTOCELL to vary its resistance?
4. What part of the PHOTOCELL is sensitive to light? 5. Does an LED have polarity?
6. What will cause the resistance of the PHOTOCELL to increase?
7. This circuit has how many electronic parts?
8. What do you use to shield the light from hitting the PHOTOCELL?
9. This circuit has an LED, a _____, and a BATTERY.
10. True or False, an LED is sensitive to light?

**QUICK-CHECK ANSWER KEY for Experiment 03 QUIZ
for Mr Circuit Electronics Training (“How a PHOTOCCELL Works”)**

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

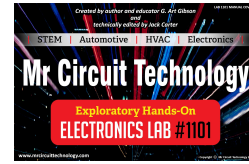Count the right answers and record the score of right answers in your grade book.



<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p>#1 How many leads does a Photocell have?</p> <p>A. 1 B. 2 C. 3 D. 6</p>	<p>#6 This circuit has three components. They are the battery snap, a resistor, and a _____.</p> <p>A. Photocell B. Potentiometer C. capacitor D. microphone</p>	<p>A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p>#2 Does a Photocell have polarity?</p> <p>A. YES B. NO C. maybe D. not necessarily</p>	<p>#7 In this experiment, what do we use to shield the light from hitting the Photocell?</p> <p>A. a flashlight B. a fork C. a hand D. a forklift</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p>#3 In order for a Photocell to vary its resistance, light has to hit the _____.</p> <p>A. top surface B. bottom surface C. the leads D. the left side</p>	<p>#8 A Photocell changes its resistance because it is sensitive to _____.</p> <p>A. air B. pressure C. gravity D. light</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>	<p>#4 If you reverse the leads on the battery snap, how will that affect the circuit?</p> <p>A. the LED will be brighter B. the circuit will work just fine C. the LED will get hot and burn up D. the LED will not light up</p>	<p>#9 When you block the amount of light hitting a Photocell, its resistance _____.</p> <p>A. is not affected B. decreases C. causes more capacitance in the circuit D. increases</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p>#5 If you put this circuit into a dark room, how will that affect the LED brightness?</p> <p>A. it will be super bright B. it will burn out C. it will be dimmer D. it will be the same as in bright light</p>	<p>#10 How does the brightness of the light that hits the Photocell affect the LED in the circuit?</p> <p>A. has no effect at all B. brighter the light, brighter the LED C. LEDs don't get brighter or dimmer D. dimmer the light, brighter the LED</p>	<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>

BUILD A BETTER FUTURE by UNDERSTANDING SCIENCE-ELECTRONICS



PHOTOCELLS VARY CURRENT WITH LIGHT



BASIC ELECTRONICS LAB 1

“HOW A PHOTOCELL WORKS”

(Poster MC1-03-P01)

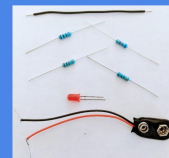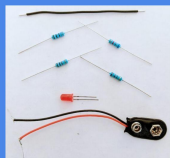

PRICE LIST May 2024

P
R
I
C
E
L
I
S
T

PARTS KIT	Mr Circuit Series 1	Price
Number	SCIENCE / ELECTRONICS "PARTS KITS"	Each
MC1-00-PK	Solderless Circuit Board to build kits	\$3.95
MC1-01-PK	Parts Kit for "How a Resistor Works	\$1.95
MC1-02-PK	Parts Kit for "How a Potentiometer Works	\$2.95
MC1-03-PK	Parts Kit for "How a Photocell Works	\$1.95
MC1-04-PK	Parts Kit for "How a Capacitor Works	\$2.95
MC1-05-PK	Parts Kit for "How a Speaker Works	\$2.95
MC1-06-PK	Parts Kit for "How a Diode Works	\$1.95
MC1-07-PK	Parts Kit for "How an SCR Works	\$3.95
MC1-08-PK	Parts Kit for "How an NPN Transistor Works	\$2.95
MC1-09-PK	Parts Kit for "How a PNP Transistor Works	\$2.95
MC1-10-PK	Parts Kit for "How a Transistor Oscillator Works	\$3.95
MC1-11-PK	Parts Kit for "How a 555 Timer IC Works	\$2.95
MC1-12-PK	Parts Kit for "Burglar Alarm circuit	\$3.95
MC1-13-PK	Parts Kit for "Solar-Activated Night Light circuit	\$3.95
MC1-14-PK	Parts Kit for "DC to DC Power Supply circuit	\$2.95
MC1-15-PK	Parts Kit for "Electronic Metronome circuit	\$4.95
MC1-16-PK	Parts Kit for "Electronic Motorcycle circuit	\$3.95
MC1-17-PK	Parts Kit for "Railroad Lights circuit	\$2.95
MC1-18-PK	Parts Kit for "Variable Speed Lights circuit	\$3.95
MC1-19-PK	Parts Kit for "Continuity Tester circuit	\$4.95
MC1-20-PK	Parts Kit for "Audio Generator circuit	\$5.95
MC1-21-PK	Parts Kit for "Electronic Police Siren circuit	\$4.95
MC1-22-PK	Parts Kit for "Solar-Activated Wake-Up Alarm circuit	\$3.95
MC1-23-PK	Parts Kit for "Variable Timer circuit	\$3.95
MC1-24-PK	Parts Kit for "Moisture Detector circuit	\$2.95
MC1-25-PK	Parts Kit for "Code Oscillator circuit	\$4.95
MC1-26-PK	Parts Kit for "Audible Water Detector circuit	\$4.95
MC1-27-PK	Parts Kit for "English Police Siren circuit	\$4.95
MC1-28-PK	Parts Kit for "Electronic Canary circuit	\$7.95
MC1-29-PK	Parts Kit for "fantasy Space Machine Gun circuit	\$5.95
MC1-30-PK	Parts Kit for "Ultrasonic Pest Repeller circuit	\$5.95
Set-MC1-PK	Complete Set of All Series 1 Parts Kits (31 total)	\$120.00