

For more info:

www.MrCircuitTechnology.com

Gary@MrCircuitTechnology.com

Mr Circuit Technology

Science/Electronics Experiment Kits and Labs


“HOW A CAPACITOR WORKS”

LESSON PLAN

Table of Contents

- Page 01 - Explanation of the Experiment
- Page 02 - Purpose of the Experiment and Parts Needed
- Page 03 - Do the Experiment (part 1 of 3)
- Page 04 - Do the Experiment (part 2 of 3)
- Page 05 - Do the Experiment (part 3 of 3)
- Page 06 - Crossword Puzzle
- Page 07 - Word Search Puzzle
- Page 08 - Written 10-Question Multiple Choice Quiz
- Page 09 - Answers to Crossword
- Page 10- Answers to Word Search
- Page 11 - Answer Key to Written Quiz
- Page 12 - Poster to put up on classroom wall
- Page 13 - Price List for Parts Kits for your to order more. Send Purchase Order to Gary@MrCircuitTechnology.com or order online at www.MrCircuitTechnology.com

Experiment Parts Kit
#MC1-00-PK
 Solderless
 Circuit Board
 Exciting, Educational
 and Fun



Experiment Parts only
 (packaged in a 3x5 inch
 resealable plastic bag.)

**LEARN more today,
 EARN more tomorrow!**


Copyright © Mr Circuit Technology 2024

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com

Science/Electronics Kits and Labs

Mr Circuit Technology

Science Experiment Kit
#MC1-04
 “How a
 Capacitor
 Works”
 Exciting, Educational
 and Fun



**LEARN more today,
 EARN more tomorrow!**

To get started, go to www.MrCircuitTech.com
 and click on Mr Circuit Lab 1 button and
 then, on the menu, click on Experiment 4
 “How A Capacitor Works” and then follow
 the instructions given by the online
 presentation. Enjoy this hands-on way to
 learn science and electronics!

Copyright © Mr Circuit Technology 2024


MSRP \$3.95

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com


Science/Electronics Kits and Labs

Mr Circuit Technology

Mr Circuit Lab 1 - Experiment 04

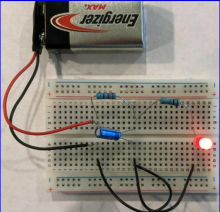

How a Capacitor Works - 10 uF

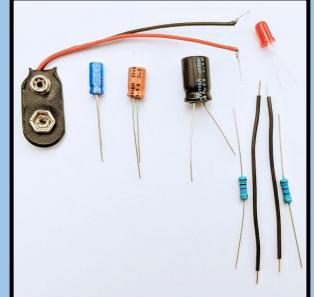

PREPARATION: You can put the Page 12 poster up on your classroom wall to announce the fact that you are going to do the Science-Electronics Experiment.

Step 1 - Make a copy of pages 1 through 8 for each student. The students can read and do these pages on their own or you can guide them.

Step 2 - Hand out Parts Kit #MC1-00-PK (that has the Solderless Circuit Board) and Parts Kit #MC1-04-PK (that has the experiment parts) with a 9-Volt battery. Give these items to each student along with the 8 pages.

Step 3 - When your students have completed the experiment, collect all the Parts Kits and batteries for later use.

Step 4 - Collect all the Written Quizzes for grading and use the Answer Key to grade them.

For Tech Support or any questions, you can email us or call 805-295-1642

EXPLANATION OF EXPERIMENT

*** You are going to build a circuit to observe a CAPACITOR storing an electrical charge.


Here is the SCHEMATIC DIAGRAM of the circuit you will build.

The symbol (with a squiggly line) represents a RESISTOR.

1

2

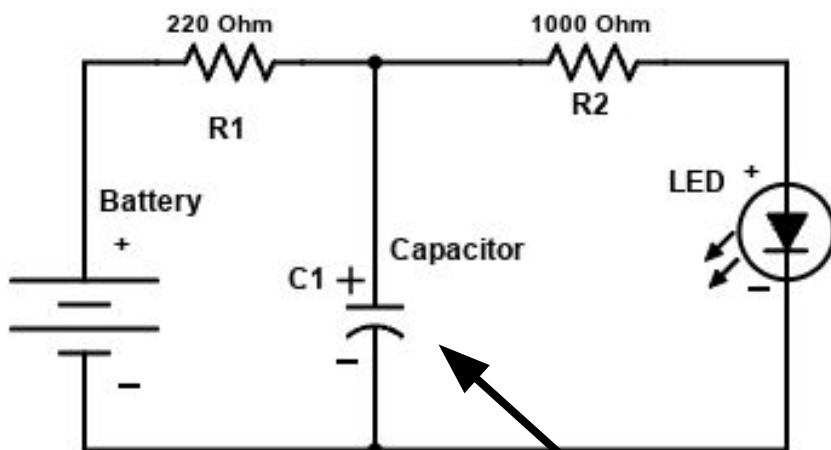The LED symbol (a circle with an arrow in it) represents a light-emitting diode that lights up when electric current is flowing through it.



3

This curved line and straight line with a plus and minus is an ELECTROLYTIC CAPACITOR.

The electron current in this circuit flows out of the negative side of the battery to the LED and to the CAPACITOR, then through the RESISTORS back to the positive side of the battery.

(Continue to Page 2)

PURPOSE OF THIS EXPERIMENT

*** To observe CAPACITORS storing and discharging electrical charge..


PARTS NEEDED FOR EXPERIMENT

In this experiment, you will use a BATTERY SNAP




three ELECTROLYTIC CAPACITORS

1000 uF

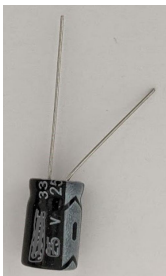

100 uF

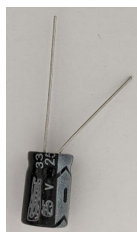

10 uF



uF = MicroFarad is a measurement of capacitance.


an LED



two Jumper Wires



and a SOLDERLESS CIRCUIT BOARD.

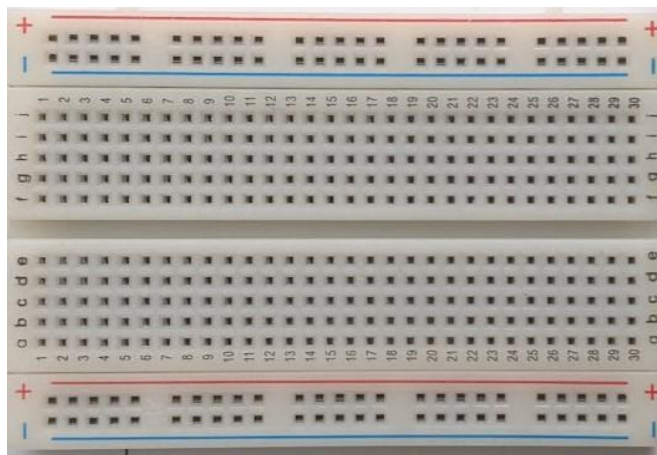


You will also need a good 9 Volt battery
(Continue to Page 3)

DO THE EXPERIMENT (part 1 of 3)

MC1-04-R-3

*** You are going to build a circuit to demonstrate CAPACITORS storing and discharging an electrical charge.

Step 1 - Take out a Battery Snap and install it with its Red lead in hole 9g and its Black lead in hole 9d as shown in the pictorial diagram. (Note: If you reverse the leads, the circuit will NOT work.)

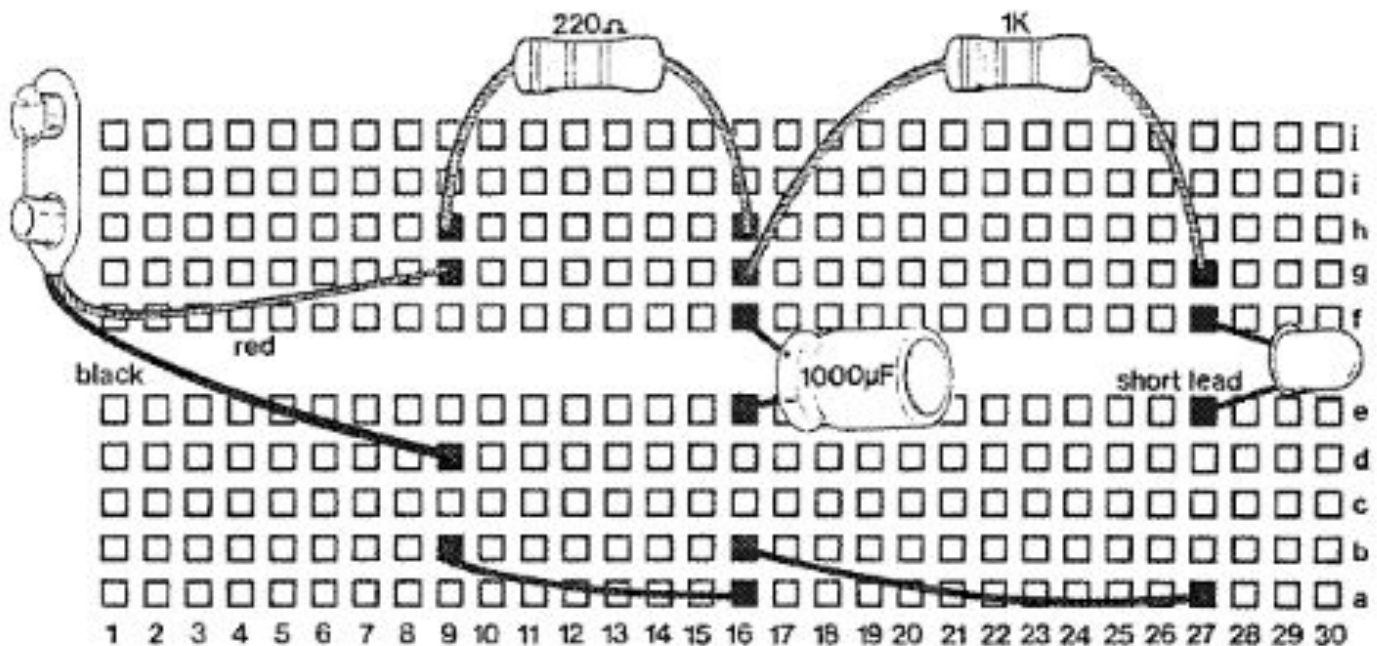PICTORIAL DIAGRAM

Step 2 - Install an LED with its short lead into hole 27e and its long lead into hole 27f.

Step 3 - Install a 220 Ohm resistor (color bands Red, Red, Brown, Gold) as shown on the pictorial into holes 9h and 16h.


(Continue to Page 4)

DO THE EXPERIMENT (part 2 of 3)

MC1-04-R-4

Step 4 - Install a 1000 Ohm (1k) RESISTOR (color bands Brown, Black, Red, Gold) as shown on the pictorial into holes 16g and 27g.

Step 5 - Install a Jumper Wire into holes 9b to 16a and another Jumper Wire into holes 16b to 27a.

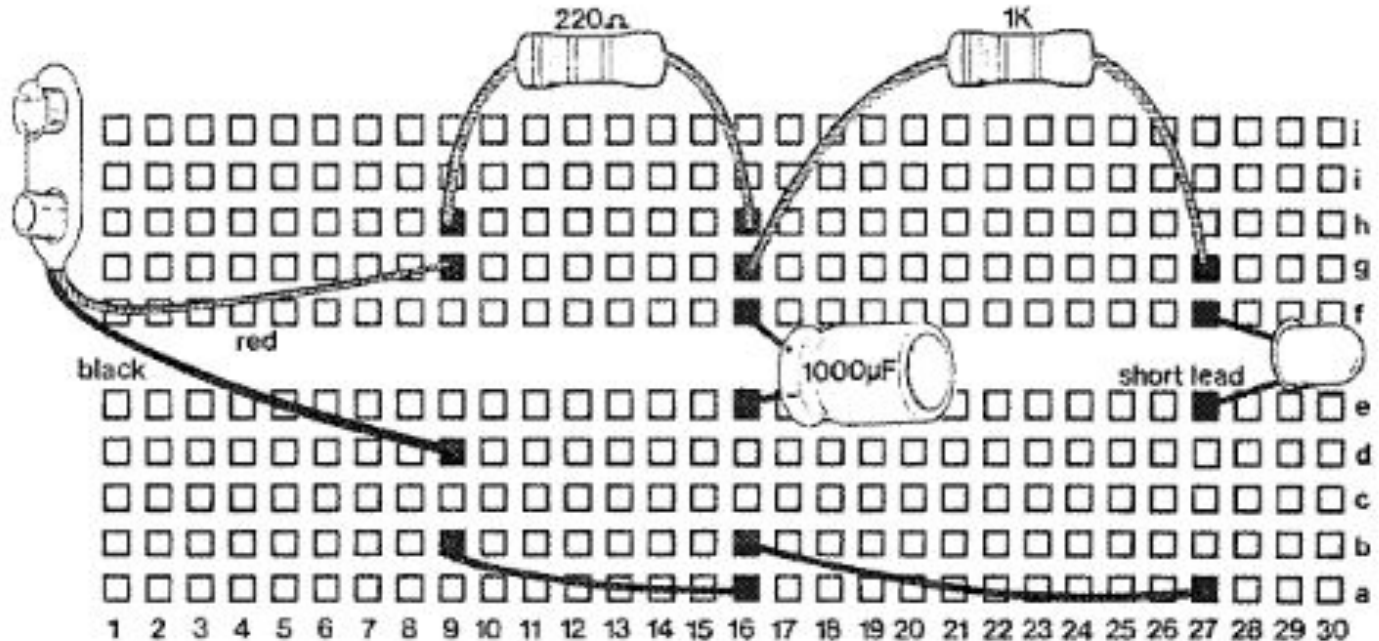PICTORIAL DIAGRAM

Step 6 - Now touch the 9V battery to the battery snap and observe that the LED lights up. Then, when you disconnect the battery, the LED remains lit for short time while the CAPACITOR is discharging. The LED shuts off when the CAPACITOR is discharged. Try it again and notice how long the LED remains lit after you disconnect the battery.

(Continue to Page 5)

DO THE EXPERIMENT (part 3 of 3)

Step 7 - Now remove the 1000 μ F CAPACITOR and put a 100 μ F CAPACITOR in its place in the circuit.

Step 8 - Now touch the 9V battery to the battery snap and observe that the LED lights up. Then, when you disconnect the battery, the LED remains lit for very short time while the CAPACITOR is discharging.

Step 8 - Now remove the 100 μ F CAPACITOR and put a 10 μ F CAPACITOR in its place in the circuit.

Step 9 - Now touch the 9V battery to the battery snap and observe that the LED lights up. Then, when you disconnect the battery, the LED remains lit for SUPER short time while the CAPACITOR is discharging. You may not even see the LED remain lit at all because the time is so short.


CONCLUSION

*** You should have observed that a CAPACITOR can store an electrical charge which can be used to keep an LED lit for a short time after the 9 Volt power is removed from the circuit. Capacitors are used in all kinds of timing circuits in electronics.

(End of Experiment 4)

CROSSWORD

Experiment 4 - "How a CAPACITOR Works"

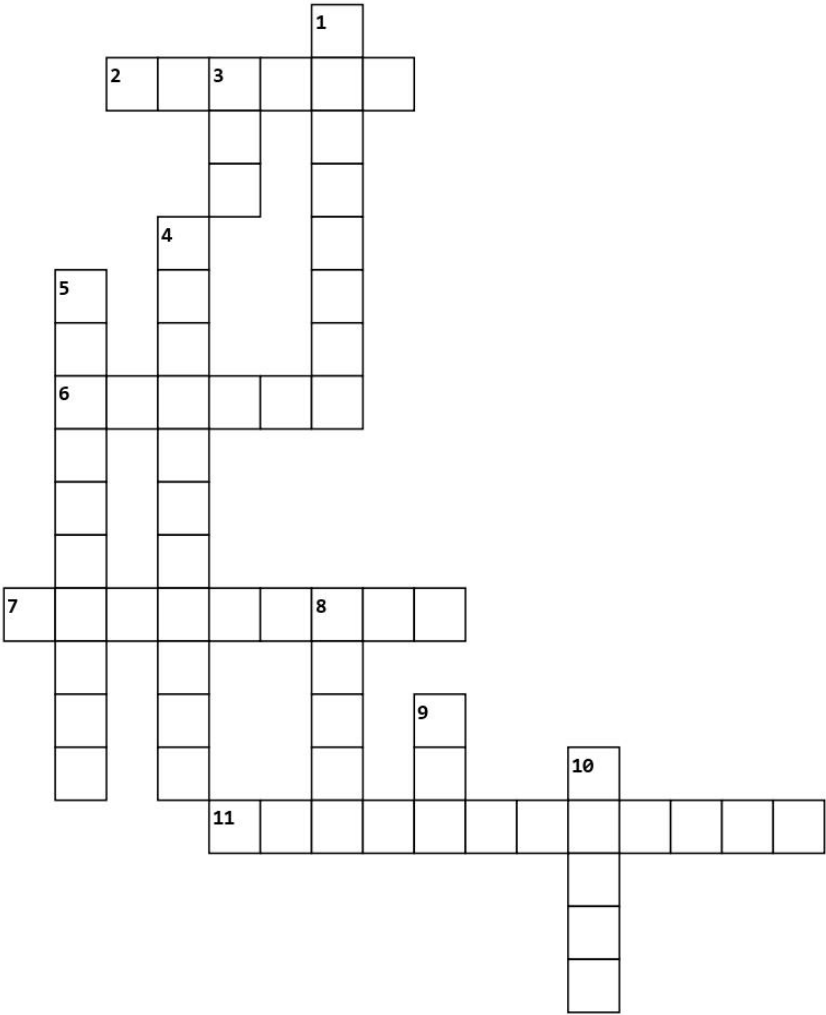

Across

- 2. If we want the LED to remain lit longer, we have to use a _____ capacitor.
- 6. A capacitor can store a _____ .
- 7. What keeps the LED lit for a short time when you remove power from the circuit?
- 11. What kind of capacitor are we using in this experiment?

Down

- 1. The short lead on the LED is connected toward the _____ of the battery.
- 3. What is the second color band on a 220 Ohm resistor?
- 4. The larger the _____ the longer the LED will remain lit?
- 5. What does this stand for uF ?
- 8. How many sizes of capacitor did we use in this experiment?
- 9. If we reverse the battery leads, the LED will _____ light up.
- 10. What is the second color band on a 1000 Ohm resistor?

Experiment 4 - "How a CAPACITOR Works"


J R D F H H L H Q X G F A P W U A D D H
 U E O Z L S M J B L W T I K N M O A P Q
 M D C R K L O Z E X M R M R T V C Y N T
 S P N T T T B X W U I X P E Z I L L T W
 D X V Q D B R V O Y C T E G V H L V K M
 V D Y Y Z S G C T Q R C L R L D H Z R S
 G F M U W P K N V M O A E A Q H N X P X
 K C C Y Y N J B V M F P C L B E R T B A
 I D N A T J E N B S A A T J G F A H X K
 W T O T P U N U N U R C R E D G S R J A
 V N T F U A Y W E X A I O P O N I E P C
 C L H J I O C S G Q D T L N R H Q E S A
 F L G X E D S I A O T O Y C V Q L N S M
 A D B R P B X U T I E R T Q H B B E M W
 Z U R L T R N D I A X M I O E X G G G J
 G T S W A D R T V Q N M C F B L T F W K
 J T N Q V C D Z E R C C O Y L Q N E O L
 H B A S F P K H Y I Q P E E E R T F C O
 Q P L O P F D I U R S Z I X Z D G S X R
 R G W X F V C H A R G E B E E Q L W C P

1. What does uF this stand? 2. What is the second color band on a 220 Ohm resistor?
3. What is the second color band on a 1000 Ohm resistor?
4. What keeps the LED lit for a short time when you remove power from the circuit?
5. The larger the _____ the longer the LED will remain lit?
6. What kind of capacitor are we using in this experiment?
7. If we reverse the battery leads, the LED will _____ light up.
8. If we want the LED to remain lit longer, we have to use a _____ capacitor.
9. A capacitor can store a _____ .
10. The short lead on the LED is connected toward the _____ of the battery.
11. How many sizes of capacitor did we use in this experiment?




QUIZ for Exp 04 or STEM KIT #04 in the Mr Circuit Electronics Training Lab 1

(Page 8)

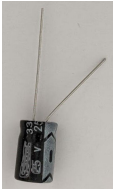

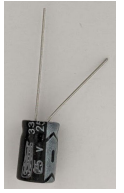This Quiz covers the training learned by completing “How a Capacitor Works” Experiment 4



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A
B
C
D

#1 In Experiment #4, what is the component that you learned about?
A. a capacitor
B. a resistor
C. an LED
D. a battery snap

#6 What happens to the LED if we reverse the polarity on the battery?
A. it lights up just fine
B. it burns out the LED
C. the LED will not light up
D. the LED will get hot

A
B
C
D

A
B
C
D

#2 In Exp. #4, how many resistors do we use?
A. 1
B. 2
C. 3
D. 4

#7 The more capacitance a capacitor has, the _____ electrical charge it will hold.
A. less
B. fuzzier
C. worse
D. more

A
B
C
D

A
B
C
D

#3 In Exp. #4, when you disconnect the battery, the LED remains lit for a time because _____.
A. the two resistors keep it lit
B. the energy stored in the capacitor keeps it lit
C. LEDs store electrons
D. your eyes are playing tricks on you.

#8 Which value of capacitor will hold more electrical charge?
A. 1000uF
B. 100uF
C. 10uF
D. 1uF

A
B
C
D

A
B
C
D

#4 What happens to the LED when we reduce the value of the capacitor in the circuit and then disconnect the battery?
A. The LED remains lit for a longer time.
B. The LED will burn out.
C. The LED remains lit for shorter time.
D. It will have no effect on the LED.

#9 What is the purpose of a capacitor in a circuit?
A. to vary the resistance
B. to store inductance
C. to store an electrical charge
D. to increase the wattage

A
B
C
D

A
B
C
D

#5 In Exp. #4, what type of capacitor are we using?
A. an electrolytic capacitor
B. a ceramic disc capacitor
C. a polyester film capacitor
D. a variable capacitor


#10 Does the capacitor in this circuit have polarity?
A. NO
B. can't tell
C. YES
D. its an inductor

A
B
C
D

Score	
-------	--

ANSWERS FOR CROSSWORD

Experiment 4 - "How a CAPACITOR Works"

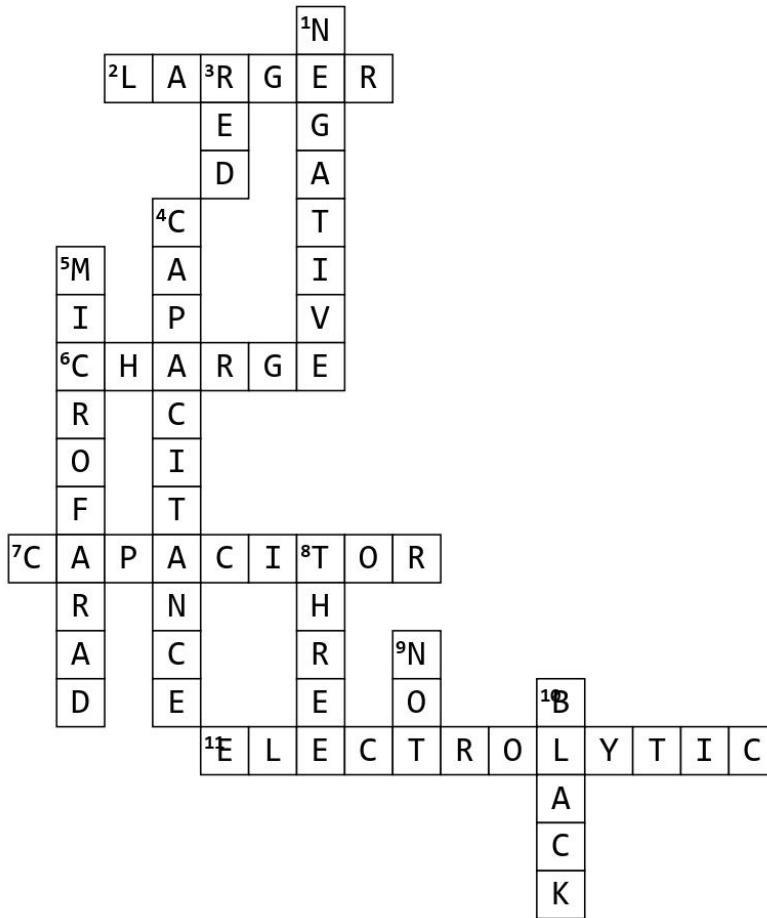

Across

- 2. If we want the LED to remain lit longer, we have to use a _____ capacitor.
- 6. A capacitor can store a _____ .
- 7. What keeps the LED lit for a short time when you remove power from the circuit?
- 11. What kind of capacitor are we using in this experiment?

Down

- 1. The short lead on the LED is connected toward the _____ of the battery.
- 3. What is the second color band on a 220 Ohm resistor?
- 4. The larger the _____ the longer the LED will remain lit?
- 5. What does this stand for uF ?
- 8. How many sizes of capacitor did we use in this experiment?
- 9. If we reverse the battery leads, the LED will _____ light up.
- 10. What is the second color band on a 1000 Ohm resistor?

ANSWERS FOR WORD SEARCH

Experiment 4 - "How a CAPACITOR Works"


J	R	D	F	H	H	L	H	Q	X	G	F	A	P	W	U	A	D	D	H
U	E	O	Z	L	S	M	J	B	L	W	T	I	K	N	M	O	A	P	Q
M	D	C	R	K	L	O	Z	E	X	M	R	M	R	T	V	C	Y	N	T
S	P	N	T	T	B	X	W	U	I	X	P	E	Z	I	L	L	T	W	
D	X	V	Q	D	B	R	V	O	Y	C	T	E	G	V	H	L	V	K	M
V	D	Y	Y	Z	S	G	C	T	Q	R	C	L	R	L	D	H	Z	R	S
G	F	M	U	W	P	K	N	V	M	O	A	E	A	Q	H	N	X	P	X
K	C	C	Y	Y	N	J	B	V	M	F	P	C	L	B	E	R	T	B	A
I	D	N	A	T	J	E	N	B	S	A	A	T	J	G	F	A	H	X	K
W	T	O	T	P	U	N	U	N	U	R	C	R	E	D	G	S	R	J	A
V	N	T	F	U	A	Y	W	E	X	A	I	O	P	O	N	I	E	P	C
C	L	H	J	I	O	C	S	G	Q	D	T	L	N	R	H	Q	E	S	A
F	L	G	X	E	D	S	I	A	O	T	O	Y	C	V	Q	L	N	S	M
A	D	B	R	P	B	X	U	T	I	E	R	T	Q	H	B	B	E	M	W
Z	U	R	L	T	R	N	D	I	A	X	M	I	O	E	X	G	G	G	J
G	T	S	W	A	D	R	T	V	Q	N	M	C	F	B	L	T	F	W	K
J	T	N	Q	V	C	D	Z	E	R	C	C	O	Y	L	Q	N	E	O	L
H	B	A	S	F	P	K	H	Y	I	Q	P	E	E	E	R	T	F	C	O
Q	P	L	O	P	F	D	I	U	R	S	Z	I	X	Z	D	G	S	X	R
R	G	W	X	F	V	C	H	A	R	G	E	B	E	E	Q	L	W	C	P

1. What does uF this stand? 2. What is the second color band on a 220 Ohm resistor?
3. What is the second color band on a 1000 Ohm resistor?
4. What keeps the LED lit for a short time when you remove power from the circuit?
5. The larger the _____ the longer the LED will remain lit?
6. What kind of capacitor are we using in this experiment?
7. If we reverse the battery leads, the LED will _____ light up.
8. If we want the LED to remain lit longer, we have to use a _____ capacitor.
9. A capacitor can store a _____ .
10. The short lead on the LED is connected toward the _____ of the battery.
11. How many sizes of capacitor did we use in this experiment?

**QUICK-CHECK ANSWER KEY for Experiment 04 QUIZ
for Mr Circuit Electronics Training (“How a Capacitor Works”)**

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

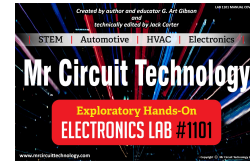
Count the right answers and record the score of right answers in your grade book.



<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p>#1 In Experiment #4, what is the component that you learned about?</p> <p>A. a capacitor B. a resistor C. an LED D. a battery snap</p>	<p>#6 What happens to the LED if we reverse the polarity on the battery?</p> <p>A. it lights up just fine B. it burns out the LED C. the LED will not light up D. the LED will get hot</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p>#2 In Exp. #4, how many resistors do we use?</p> <p>A. 1 B. 2 C. 3 D. 4</p>	<p>#7 The more capacitance a capacitor has, the _____ electrical charge it will hold.</p> <p>A. less B. fuzzier C. worse D. more</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input checked="" type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input checked="" type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p>#3 In Exp. #4, when you disconnect the battery, the LED remains lit for a time because _____.</p> <p>A. the two resistors keep it lit B. the energy stored in the capacitor keeps it lit C. LEDs store electrons D. your eyes are playing tricks on you.</p>	<p>#8 Which value of capacitor will hold more electrical charge?</p> <p>A. 1000uF B. 100uF C. 10uF D. 1uF</p>	<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>	<p>#4 What happens to the LED when we reduce the value of the capacitor in the circuit and then disconnect the battery?</p> <p>A. The LED remains lit for a longer time. B. The LED will burn out. C. The LED remains lit for shorter time. D. It will have no effect on the LED.</p>	<p>#9 What is the purpose of a capacitor in a circuit?</p> <p>A. to vary the resistance B. to store inductance C. to store an electrical charge D. to increase the wattage</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input type="radio"/> C</p> <p><input type="radio"/> D</p>	<p>#5 In Exp. #4, what type of capacitor are we using?</p> <p>A. an electrolytic capacitor B. a ceramic disc capacitor C. a polyester film capacitor D. a variable capacitor</p>	<p>#10 Does the capacitor in this circuit have polarity?</p> <p>A. NO B. can't tell C. YES D. its an inductor</p>	<p><input type="radio"/> A</p> <p><input type="radio"/> B</p> <p><input checked="" type="radio"/> C</p> <p><input type="radio"/> D</p>

BUILD A BETTER FUTURE by UNDERSTANDING SCIENCE-ELECTRONICS



CAPACITORS STORE ELECTRICAL CHARGE

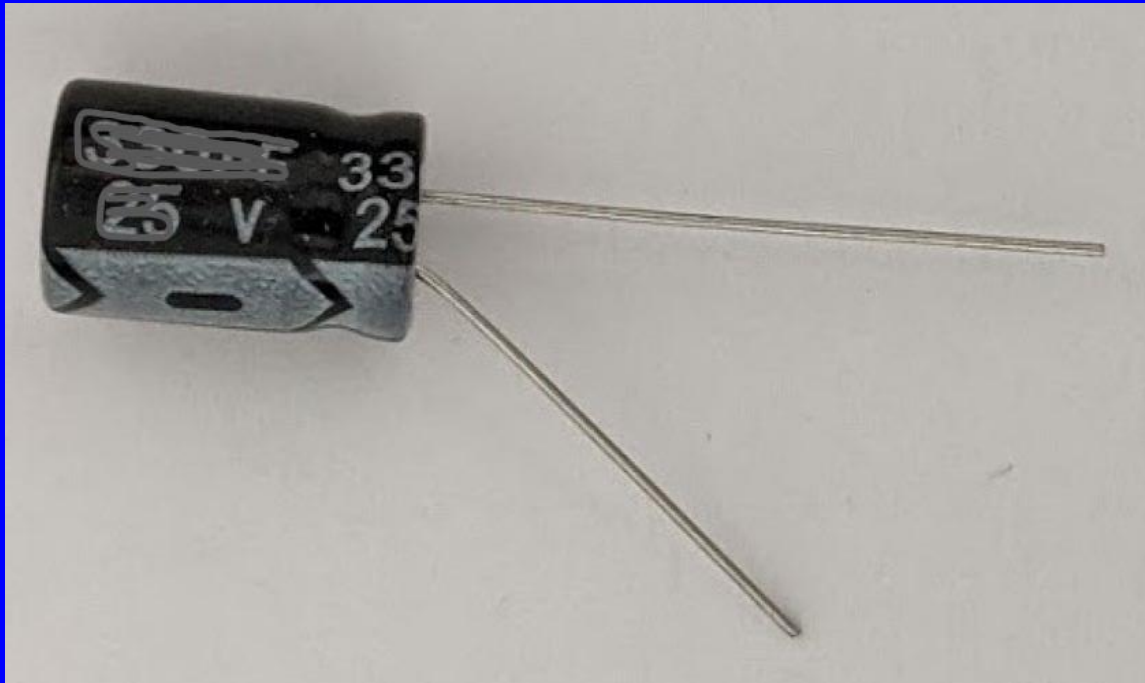

BASIC ELECTRONICS LAB 1

“HOW A CAPACITOR WORKS”

(Poster MC1-04-P01)

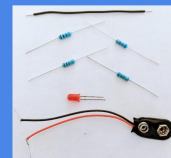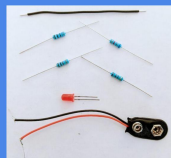

PRICE LIST May 2024

PARTS KIT	Mr Circuit Series 1	Price
Number	SCIENCE / ELECTRONICS "PARTS KITS"	Each
MC1-00-PK	Solderless Circuit Board to build kits	\$3.95
MC1-01-PK	Parts Kit for "How a Resistor Works	\$1.95
MC1-02-PK	Parts Kit for "How a Potentiometer Works	\$2.95
MC1-03-PK	Parts Kit for "How a Photocell Works	\$1.95
MC1-04-PK	Parts Kit for "How a Capacitor Works	\$2.95
MC1-05-PK	Parts Kit for "How a Speaker Works	\$2.95
MC1-06-PK	Parts Kit for "How a Diode Works	\$1.95
MC1-07-PK	Parts Kit for "How an SCR Works	\$3.95
MC1-08-PK	Parts Kit for "How an NPN Transistor Works	\$2.95
MC1-09-PK	Parts Kit for "How a PNP Transistor Works	\$2.95
MC1-10-PK	Parts Kit for "How a Transistor Oscillator Works	\$3.95
MC1-11-PK	Parts Kit for "How a 555 Timer IC Works	\$2.95
MC1-12-PK	Parts Kit for "Burglar Alarm circuit	\$3.95
MC1-13-PK	Parts Kit for "Solar-Activated Night Light circuit	\$3.95
MC1-14-PK	Parts Kit for "DC to DC Power Supply circuit	\$2.95
MC1-15-PK	Parts Kit for "Electronic Metronome circuit	\$4.95
MC1-16-PK	Parts Kit for "Electronic Motorcycle circuit	\$3.95
MC1-17-PK	Parts Kit for "Railroad Lights circuit	\$2.95
MC1-18-PK	Parts Kit for "Variable Speed Lights circuit	\$3.95
MC1-19-PK	Parts Kit for "Continuity Tester circuit	\$4.95
MC1-20-PK	Parts Kit for "Audio Generator circuit	\$5.95
MC1-21-PK	Parts Kit for "Electronic Police Siren circuit	\$4.95
MC1-22-PK	Parts Kit for "Solar-Activated Wake-Up Alarm circuit	\$3.95
MC1-23-PK	Parts Kit for "Variable Timer circuit	\$3.95
MC1-24-PK	Parts Kit for "Moisture Detector circuit	\$2.95
MC1-25-PK	Parts Kit for "Code Oscillator circuit	\$4.95
MC1-26-PK	Parts Kit for "Audible Water Detector circuit	\$4.95
MC1-27-PK	Parts Kit for "English Police Siren circuit	\$4.95
MC1-28-PK	Parts Kit for "Electronic Canary circuit	\$7.95
MC1-29-PK	Parts Kit for "fantasy Space Machine Gun circuit	\$5.95
MC1-30-PK	Parts Kit for "Ultrasonic Pest Repeller circuit	\$5.95
Set-MC1-PK	Complete Set of All Series 1 Parts Kits (31 total)	\$120.00

P
R
I
C
E
L
I
S
T