

For more
info:

www.MrCircuitTechnology.com

Gary@MrCircuitTechnology.com

Mr Circuit Technology

Science/Electronics Experiment Kits and Labs


“HOW AN SCR WORKS”

LESSON PLAN

Table of Contents

Page 01 - Explanation of the Experiment
 Page 02 - Purpose of the Experiment and Parts Needed
 Page 03 - Do the Experiment (part 1 of 3)
 Page 04 - Do the Experiment (part 2 of 3)
 Page 05 - Do the Experiment (part 3 of 3)
 Page 06 - Crossword Puzzle
 Page 07 - Word Search Puzzle
 Page 08 - Written 10-Question Multiple Choice Quiz
 Page 09 - Answers to Crossword
 Page 10- Answers to Word Search
 Page 11 - Answer Key to Written Quiz
 Page 12 - Poster to put up on classroom wall
 Page 13 - Price List for Parts Kits for your to order more. Send Purchase Order to Gary@MrCircuitTechnology.com or order online at www.MrCircuitTechnology.com

Experiment Parts Kit
#MC1-00-PK
 Solderless
 Circuit Board
 Exciting, Educational
 and Fun




Experiment Parts only
 (packaged in a 3x5 inch
 resealable plastic bag.)

**LEARN more today,
 EARN more tomorrow!**


Copyright © Mr Circuit Technology 2024

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com

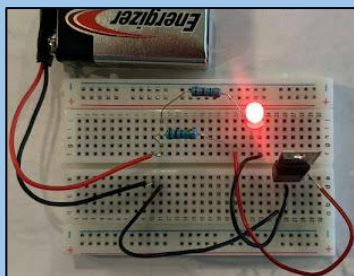Mr Circuit Technology
 Science/Electronics Kits and Labs



Science Experiment Kit
#MC1-07
 “How an SCR
 Works”
 Exciting, Educational
 and Fun



**LEARN more today,
 EARN more tomorrow!**


To get started, go to www.MrCircuitTech.com
 and click on Mr Circuit Lab #1 button and
 then, on the menu, click on Experiment 7
 “How An SCR Works” and then follow the
 instructions given by the online presentation.
 Enjoy this hands-on way to learn science and
 electronics!

MSRP \$4.95

For more info: www.MrCircuitTechnology.com
Gary@MrCircuitTechnology.com

Mr Circuit Technology
 Science/Electronics Kits and Labs

Copyright © Mr Circuit Technology 2024

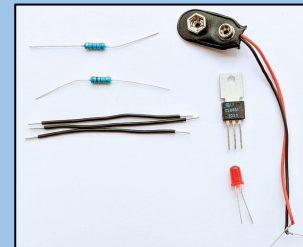

PREPARATION: You can put the Page 12 poster up on your classroom wall to announce the fact that you are going to do the Science-Electronics Experiment.

Step 1 - Make a copy of pages 1 through 8 for each student. The students can read and do these pages on their own or you can guide them.

Step 2 - Hand out Parts Kit #MC1-00-PK (that has the Solderless Circuit Board) and Parts Kit #MC1-07-PK (that has the experiment parts) with a 9-Volt battery. Give these items to each student along with the 8 pages.

Step 3 - When your students have completed the experiment, collect all the Parts Kits and batteries for later use.


Step 4 - Collect all the Written Quizzes for grading and use the Answer Key to grade them.

For Tech Support or any questions, you can email us or call 805-295-1642

EXPLANATION OF EXPERIMENT

*** You are going to build a circuit to observe that an SCR is "A DIODE WITH A DIFFERENCE" because it has an 'extra' pin called a Gate pin and will allow current to flow in one-direction only, from Cathode to Anode, only after the Gate pin has a POSITIVE voltage applied to it.

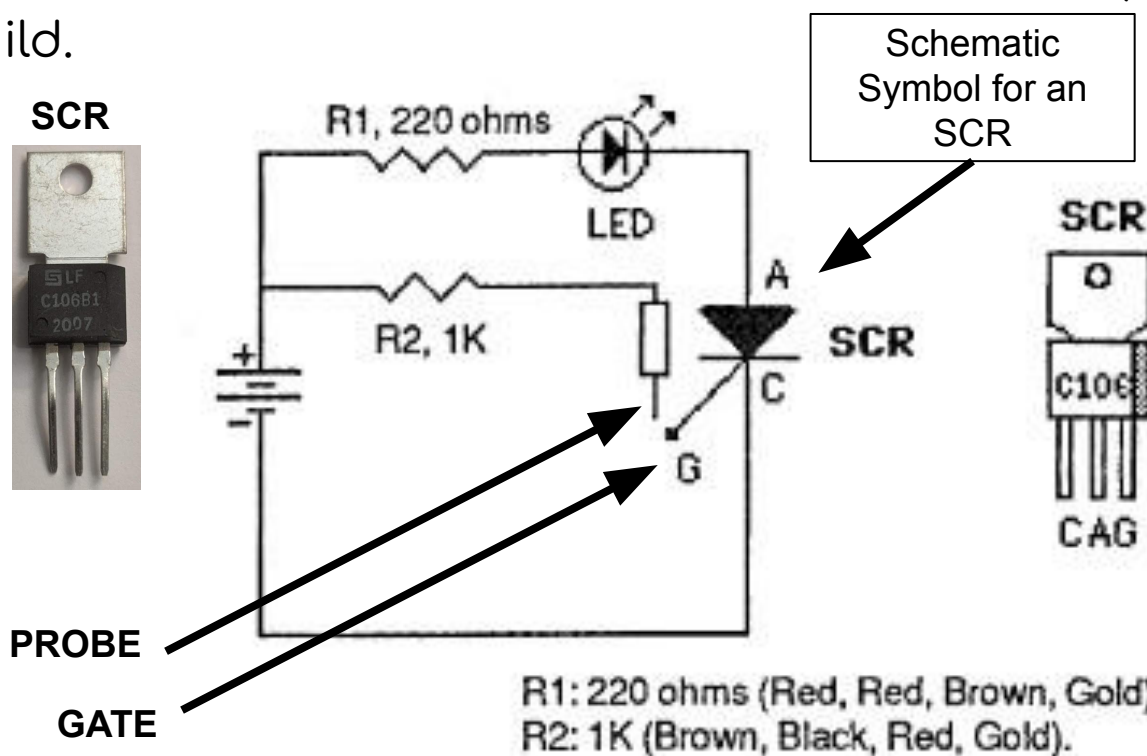Here is the SCHEMATIC DIAGRAM of the circuit you will build.



NOTE: C = Cathode pin A = Anode pin G = Gate pin

The main electron current in this circuit flows out of the negative side of the battery to the CATHODE of the SCR then through the SCR, through the LED and RESISTOR, and back to the positive side of the battery. But, no current will flow in the circuit until the PROBE wire puts a POSITIVE voltage on the Gate.

(Continue to Page 2)

PURPOSE OF THIS EXPERIMENT

*** To observe an SCR allowing current to flow in one direction only when a small voltage is put on the Gate.

PARTS NEEDED FOR EXPERIMENT

In this experiment, you will use

a BATTERY SNAP




an LED



an SCR (Silicon Control Rectifier)


This metal tab is connected to the ANODE

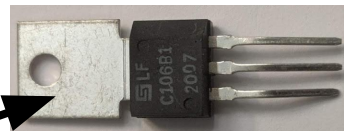


Gate
Anode
Cathode

220 Ohm resistor

1000 Ohm resistor

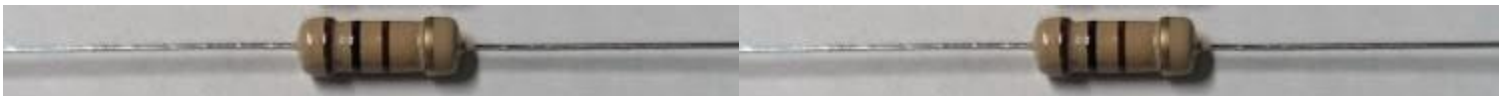

and a SOLDERLESS CIRCUIT BOARD.

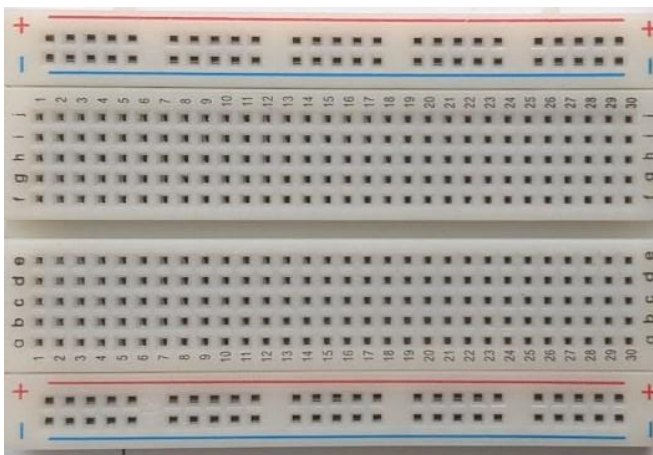

You will also need a good 9 Volt battery


(Continue to Page 3)

DO THE EXPERIMENT (part 1 of 3)

MC1-07-R-3

Now we are going to build the circuit.

Step 1 - Take out a Battery Snap and install it with its Red lead in hole 11f and its Black lead in hole 11e as shown in the pictorial diagram.

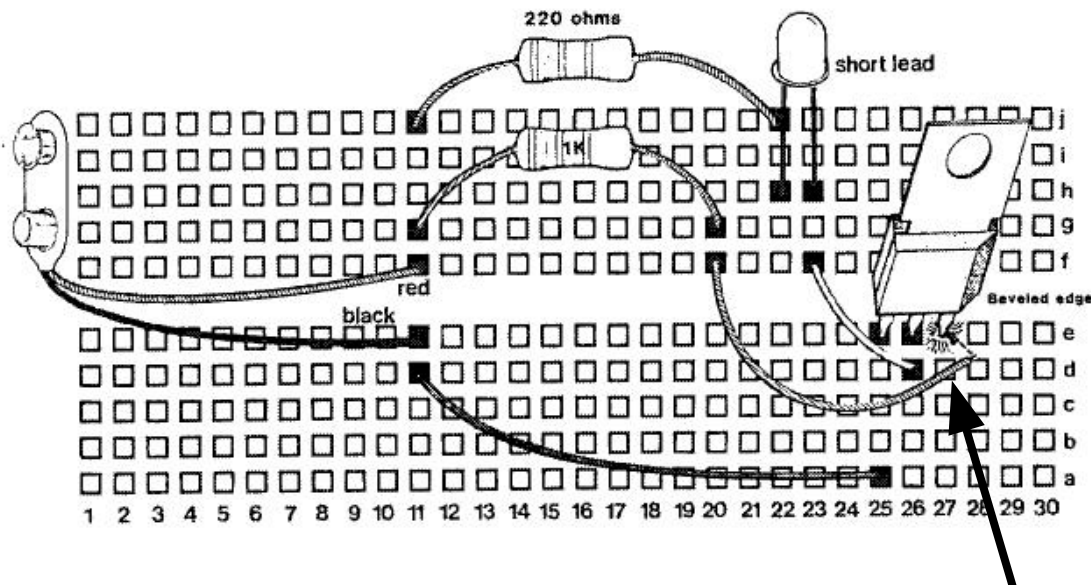**Loose Wire**

Step 2 - Install an LED with the short lead into hole 23h and the long lead into hole 22h.


Step 3 - Install a 220 Ohm resistor (color bands Red, Red, Brown, Gold) as shown on the pictorial into holes 11j and 22j. (This resistor protects the LED from too much current.)

Step 4 - Install a 1000 Ohm resistor (color bands Brown, Black, Red, Gold) into holes 11g and 20g.

(Continue to Page 4)

DO THE EXPERIMENT (part 2 of 3)

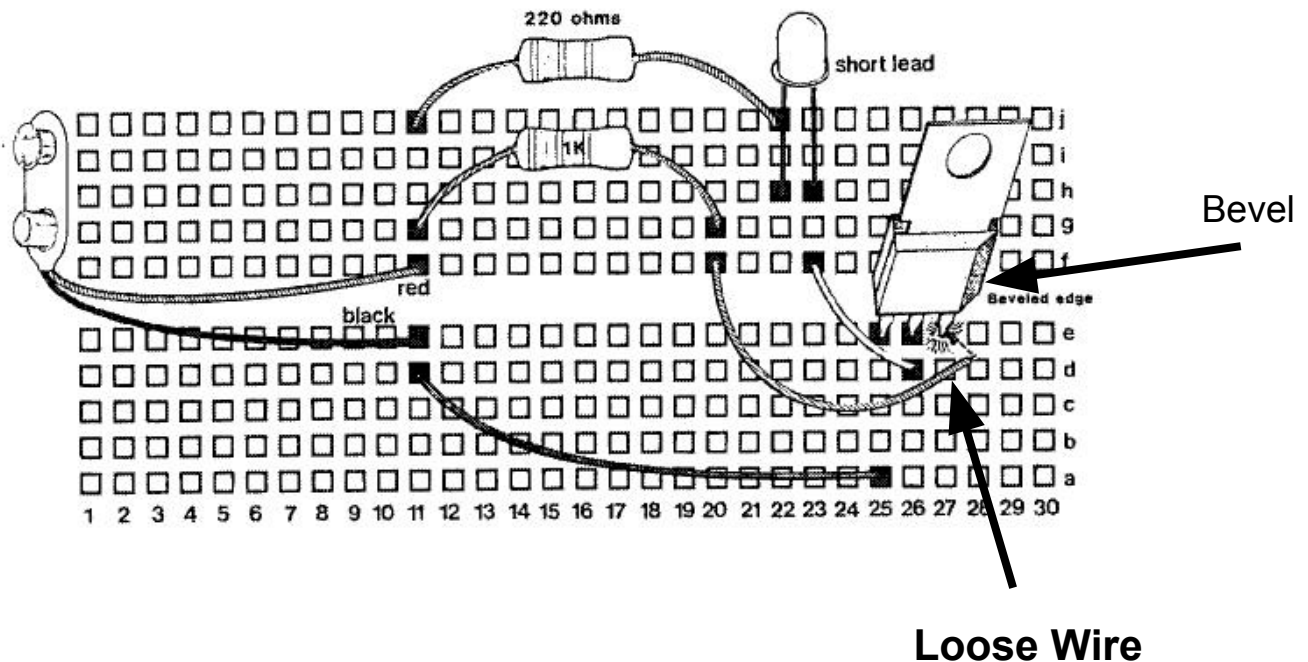Step 5 - Install the SCR in holes 25e, 26e, and 27e as shown in the pictorial with the beveled edge on the right hand side.



Step 6 - Install a Jumper Wire from hole 11d to hole 25a.

Step 7 - Install another Jumper Wire from hole 23f to 26d.

Step 8 - :Put one end of a Jumper Wire into hole 20f and leave the other end loose.

(Continue to Page 5)

DO THE EXPERIMENT (part 3 of 3)

Step 9 - Connect the BATTERY to the BATTERY SNAP. The LED should not light up..

Step 10 - Now, with the battery connected, touch the loose wire to the Gate of the SCR. (The Gate is the pin next to the beveled edge of the SCR.) You should notice the LED light up. And, even when you disconnect the wire from the Gate, the LED should remain lit.

Step 11 - The LED will remain lit until you remove power from the circuit.

To remove power from the circuit, take the black lead of the battery snap out of hole 11e. You will see the LED shut off. Then replace the black lead back into hole 11e and the LED will still not light up.

To get the LED to light up again, you have to keep the battery connected and at the same time touch the loose wire to the Gate of the SCR.


CONCLUSION

By doing this experiment, you have seen that an SCR will allow current to flow only when the Gate receives a small positive voltage. And, once the SCR is activated it will not stop the current until all power is removed from the circuit.

(End of Experiment 7)

CROSSWORD

Experiment 7 - "How an SCR Works"

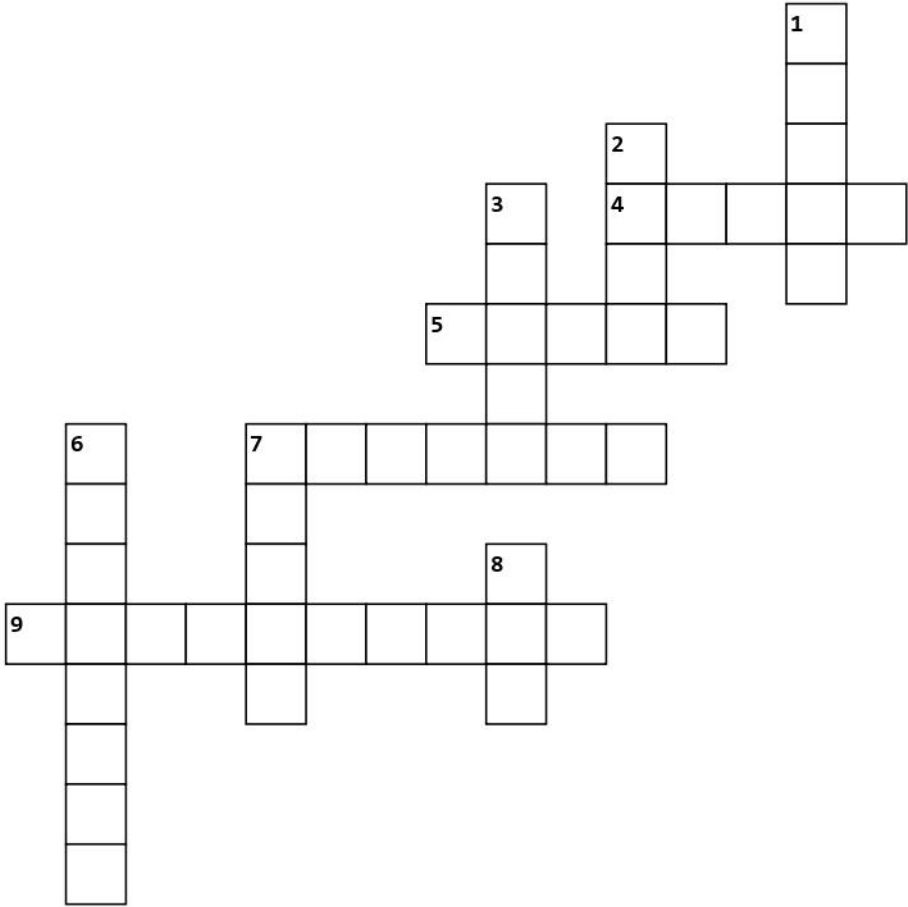

Across

- 4. The metal tab with the hole in it is connected to the _____ of the SCR.
- 5. Once an SCR is 'turned on', it remains on until the _____ is removed from the circuit.
- 7. To shut off the current through the SCR, you have to disconnect the _____ .
- 9. An SCR is a "DIODE WITH A _____ ".

Down

- 1. Because the SCR is a _____ , if you reverse the battery snap, the circuit will not conduct current.
- 2. The three pins on an SCR are the CATHODE, the ANODE, and the _____ .
- 3. The center pin on an SCR is called the _____ .
- 6. To 'trigger' the SCR, a _____ voltage has to be applied to the GATE.
- 7. The GATE pin on the SCR is marked by the _____ .
- 8. What is the abbreviation for SILICON CONTROL RECTIFIER?

Experiment 7 - "How an SCR Works"

S D Q W J Y G X E M N U R W F K K L G V
L A D T V W B F F Y N Y O I Y P E Q U I
T G A T E O Q H W T K W Q P E K D F N C
S V Z X W L V R V X O Q U I M R O A M P
C X Z E V N E W B J N C C L A E N M Z G
R F P D R D Q E E H P Z D L J N A D P V
A A H G X L E Q V G H Q L A I D H X L M
V A K K Z N J P E I T A Q W N O N V C E
X N W K K X K C L V P Z F L G Q I Y M A
K O L B Q C L O K V R U G U F O I U Q D
K D Q S O J S W K I A N U K D G Y Z B J
P E H N Z I Z S Z R J J E R I C Q R A Q
U P S K V Y H S N E I O P O F U M L T O
J P O S I T I V E D P O V A F Z K K T T
Z N A U K I L G W R I Z E T E M C L E Y
U H L R P O W E R V W T D C R O N P R O
F B Z M M O H B I U I R O O E P L H Y A
W A V X N M E R Z Q G W I Z N U L U S X
S O E W M V R P Y E Q Z D R C Q K U E J
F E N J A Y O R I Z M L B A E K A F B M

1. What is the abbreviation for SILICON CONTROL RECTIFIER?
2. The three pins on an SCR are the CATHODE, the ANODE, and the _____.
3. The center pin on an SCR is called the _____.
4. Once an SCR is 'turned on', it remains on until the _____ is removed from the circuit.
5. The GATE pin on the SCR is marked by the _____.
6. The metal tab with the hole in it is connected to the _____ of the SCR.
7. To shut off the current through the SCR, you have to disconnect the _____.
8. Because the SCR is a _____, if you reverse the battery snap, the circuit will not conduct current.
9. To 'trigger' the SCR, a _____ voltage has to be applied to the GATE.
10. An SCR is a "DIODE WITH A _____".



QUIZ for Exp 07 or STEM KIT #07 in the Mr Circuit Electronics Training Lab 1

This Quiz covers the training learned by completing

“How an SCR (Silicon Control Rectifier) Works” Exp. 7



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A #1 What are the three connections on an SCR?
B A. Input, Output, and Neutral
C B. Up, Down, Middle
D C. Right, Left, Straight
D D. Cathode, Anode, Gate

#6 The letters SCR in Exp. #7 stand for ‘Silicon Controlled Rectifier’. How many connection leads does an SCR have?
A. 5
B. 4
C. 3
D. 2

A #2 Once an SCR is turned on, in order to turn it off, you need to _____.
B A. remove the voltage on the Gate
C B. clap your hands
D C. remove the power from the entire circuit
D D. double the voltage

#7 If a positive voltage is applied to the Gate of an SCR, what happens in the circuit?
A. the electrons flow through the SCR
B. the SCR will turn off
C. the resistance of the SCR increases
D. absolutely nothing

A #3 Most of the electron current flowing through an SCR is flowing through the _____.
B A. Anode to Cathode circuit
C B. the Gate circuit
D C. Anode to Gate circuit
D D. Cathode to Anode circuit

#8 The Anode lead is connected internally to the _____ on the SCR.
A. metal tab with a hole in it
B. to the Gate lead
C. to the Cathode lead
D. to the round edge on the SCR

A #4 To turn on an SCR in a circuit, you need a _____.
B A. large current on the Gate
C B. small positive voltage on the Anode
D C. small positive voltage on the Gate
D D. large current on the Cathode

#9 If we reverse the polarity of the battery snap in the circuit, what will happen?
A. it will not work
B. it will work just fine
C. the SCR will burn out
D. the LED will self-destruct


A #5 The Gate lead on the SCR in this experiment is marked by the _____.
B A. metal tab on the SCR
C B. left lead on the SCR
D C. beveled edge on the SCR
D D. center lead on the SCR

#10 An SCR is considered to be a _____.
A. a variable resistor
B. a variable capacitor
C. “a diode with a difference”
D. a good potentiometer

Score []

ANSWERS FOR CROSSWORD

Experiment 7 - "How an SCR Works"

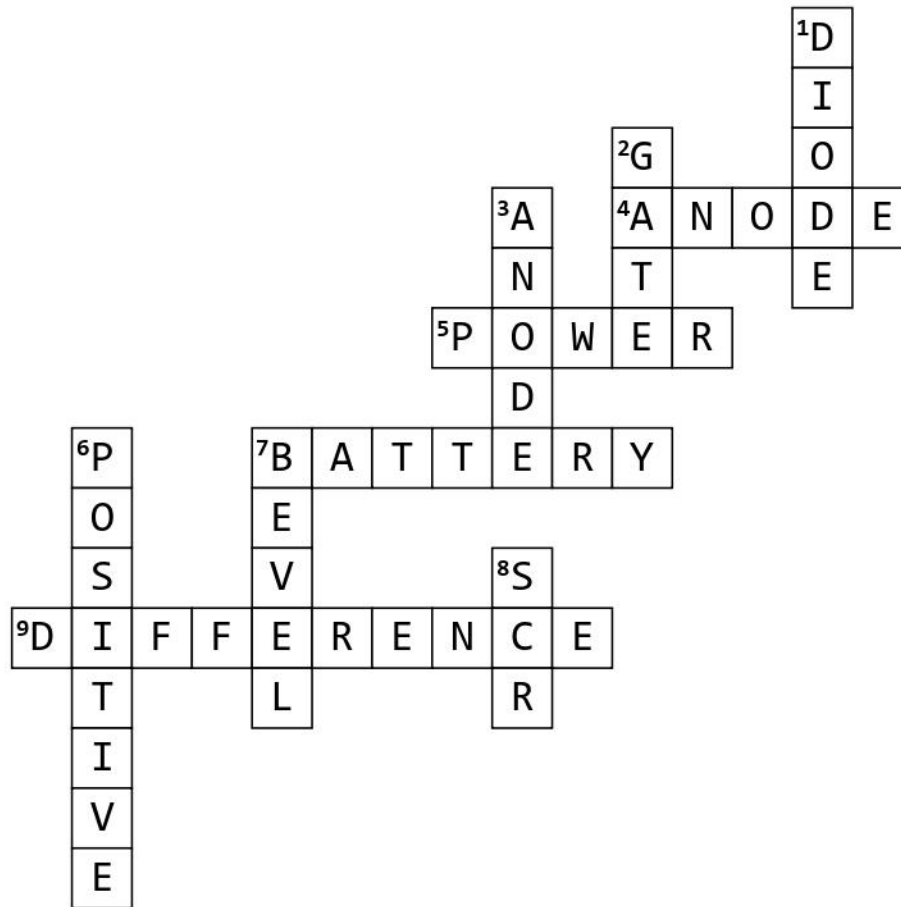

Across

- The metal tab with the hole in it is connected to the _____ of the SCR.
- Once an SCR is 'turned on', it remains on until the _____ is removed from the circuit.
- To shut off the current through the SCR, you have to disconnect the _____.
- An SCR is a "DIODE WITH A _____".

Down

- Because the SCR is a _____, if you reverse the battery snap, the circuit will not conduct current.
- The three pins on an SCR are the CATHODE, the ANODE, and the _____.
- The center pin on an SCR is called the _____.
- To 'trigger' the SCR, a _____ voltage has to be applied to the GATE.
- The GATE pin on the SCR is marked by the _____.
- What is the abbreviation for SILICON CONTROL RECTIFIER?

ANSWERS FOR WORD SEARCH

Experiment 7 - "How an SCR Works"


S D Q W J Y G X E M N U R W F K K L G V
 L A D T V W B F F Y N Y O I Y P E Q U I
 T G A T E O Q H W T K W Q P E K D F N C
 S V Z X W L V R V X O Q U I M R O A M P
 C X Z E V N E W B J N C C L A E N M Z G
 R F P D R D Q E E H P Z D L J N A D P V
 A A H G X L E Q V G H Q L A I D H X L M
 V A K K Z N J P E I T A Q W N O N V C E
 X N W K K X K C L V P Z F L G Q I Y M A
 K O L B Q C L O K V R U G U F O I U Q D
 K D Q S O J S W K I A N U K D G Y Z B J
 P E H N Z I Z S Z R J J E R I C Q R A Q
 U P S K V Y H S N E I O P O F U M L T O
 J P O S I T I V E D P O V A F Z K K T T
 Z N A U K I L G W R I Z E T E M C L E Y
 U H L R P O W E R V W T D C R O N P R O
 F B Z M M O H B I U I R O O E P L H Y A
 W A V X N M E R Z Q G W I Z N U L U S X
 S O E W M V R P Y E Q Z D R C Q K U E J
 F E N J A Y O R I Z M L B A E K A F B M

1. What is the abbreviation for SILICON CONTROL RECTIFIER?
2. The three pins on an SCR are the CATHODE, the ANODE, and the _____.
3. The center pin on an SCR is called the _____.
4. Once an SCR is 'turned on', it remains on until the _____ is removed from the circuit.
5. The GATE pin on the SCR is marked by the _____.
6. The metal tab with the hole in it is connected to the _____ of the SCR.
7. To shut off the current through the SCR, you have to disconnect the _____.
8. Because the SCR is a _____, if you reverse the battery snap, the circuit will not conduct current.
9. To 'trigger' the SCR, a _____ voltage has to be applied to the GATE.
10. An SCR is a "DIODE WITH A _____".

QUICK-CHECK ANSWER KEY for Experiment 07 QUIZ
Mr Circuit Electronics Training (“How an SCR - Silicon Control Rectifier Works”)

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

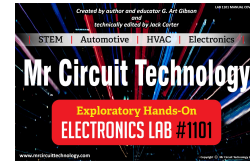Count the right answers and record the score of right answers in your grade book.



<p>A B C D</p>	<p>#1 What are the three connections on an SCR? A. Input, Output, and Neutral B. Up, Down, Middle C. Right, Left, Straight D. Cathode, Anode, Gate</p>	<p>#6 The letters SCR in Exp. #7 stand for ‘Silicon Controlled Rectifier’. How many connection leads does an SCR have? A. 5 B. 4 C. 3 D. 2</p>	<p>A B C D</p>
<p>A B C D</p>	<p>#2 Once an SCR is turned on, in order to turn it off, you need to _____ . A. remove the voltage on the Gate B. clap your hands C. remove the power from the entire circuit D. double the voltage</p>	<p>#7 If a positive voltage is applied to the Gate of an SCR, what happens in the circuit? A. the electrons flow through the SCR B. the SCR will turn off C. the resistance of the SCR increases D. absolutely nothing</p>	<p>A B C D</p>
<p>A B C D</p>	<p>#3 Most of the electron current flowing through an SCR is flowing through the _____ . A. Anode to Cathode circuit B. the Gate circuit C. Anode to Gate circuit D. Cathode to Anode circuit</p>	<p>#8 The Anode lead is connected internally to the _____ on the SCR. A. metal tab with a hole in it B. to the Gate lead C. to the Cathode lead D. to the round edge on the SCR</p>	<p>A B C D</p>
<p>A B C D</p>	<p>#4 To turn on an SCR in a circuit, you need a _____ . A. large current on the Gate B. small positive voltage on the Anode C. small positive voltage on the Gate D. large current on the Cathode</p>	<p>#9 If we reverse the polarity of the battery snap in the circuit, what will happen? A. it will not work B. it will work just fine C. the SCR will burn out D. the LED will self-destruct</p>	<p>A B C D</p>
<p>A B C D</p>	<p>#5 The Gate lead on the SCR in this experiment is marked by the _____ . A. metal tab on the SCR B. left lead on the SCR C. beveled edge on the SCR D. center lead on the SCR</p>	<p>#10 An SCR is considered to be a _____ . A. a variable resistor B. a variable capacitor C. “a diode with a difference” D. a good potentiometer</p>	<p>A B C D</p>

BUILD A BETTER FUTURE by UNDERSTANDING SCIENCE-ELECTRONICS



AN SCR (Silicon Control Rectifier)



BASIC ELECTRONICS LAB 1

“HOW AN SCR WORKS”

(Poster MC1-07-P01)

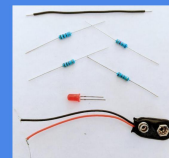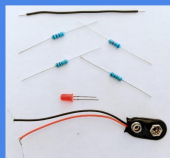

PRICE LIST May 2024

PARTS KIT	Mr Circuit Series 1	Price
Number	SCIENCE / ELECTRONICS "PARTS KITS"	Each
MC1-00-PK	Solderless Circuit Board to build kits	\$3.95
MC1-01-PK	Parts Kit for "How a Resistor Works	\$1.95
MC1-02-PK	Parts Kit for "How a Potentiometer Works	\$2.95
MC1-03-PK	Parts Kit for "How a Photocell Works	\$1.95
MC1-04-PK	Parts Kit for "How a Capacitor Works	\$2.95
MC1-05-PK	Parts Kit for "How a Speaker Works	\$2.95
MC1-06-PK	Parts Kit for "How a Diode Works	\$1.95
MC1-07-PK	Parts Kit for "How an SCR Works	\$3.95
MC1-08-PK	Parts Kit for "How an NPN Transistor Works	\$2.95
MC1-09-PK	Parts Kit for "How a PNP Transistor Works	\$2.95
MC1-10-PK	Parts Kit for "How a Transistor Oscillator Works	\$3.95
MC1-11-PK	Parts Kit for "How a 555 Timer IC Works	\$2.95
MC1-12-PK	Parts Kit for "Burglar Alarm circuit	\$3.95
MC1-13-PK	Parts Kit for "Solar-Activated Night Light circuit	\$3.95
MC1-14-PK	Parts Kit for "DC to DC Power Supply circuit	\$2.95
MC1-15-PK	Parts Kit for "Electronic Metronome circuit	\$4.95
MC1-16-PK	Parts Kit for "Electronic Motorcycle circuit	\$3.95
MC1-17-PK	Parts Kit for "Railroad Lights circuit	\$2.95
MC1-18-PK	Parts Kit for "Variable Speed Lights circuit	\$3.95
MC1-19-PK	Parts Kit for "Continuity Tester circuit	\$4.95
MC1-20-PK	Parts Kit for "Audio Generator circuit	\$5.95
MC1-21-PK	Parts Kit for "Electronic Police Siren circuit	\$4.95
MC1-22-PK	Parts Kit for "Solar-Activated Wake-Up Alarm circuit	\$3.95
MC1-23-PK	Parts Kit for "Variable Timer circuit	\$3.95
MC1-24-PK	Parts Kit for "Moisture Detector circuit	\$2.95
MC1-25-PK	Parts Kit for "Code Oscillator circuit	\$4.95
MC1-26-PK	Parts Kit for "Audible Water Detector circuit	\$4.95
MC1-27-PK	Parts Kit for "English Police Siren circuit	\$4.95
MC1-28-PK	Parts Kit for "Electronic Canary circuit	\$7.95
MC1-29-PK	Parts Kit for "fantasy Space Machine Gun circuit	\$5.95
MC1-30-PK	Parts Kit for "Ultrasonic Pest Repeller circuit	\$5.95
Set-MC1-PK	Complete Set of All Series 1 Parts Kits (31 total)	\$120.00

P
R
I
C
E
L
I
S
T