

For more info:

[www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)

[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)

# Mr Circuit Technology

Science/Electronics Experiment Kits and Labs


## Exp. 18 - "VARIABLE SPEED LIGHTS CIRCUIT"

### LESSON PLAN

#### Table of Contents

- Page 01 - Explanation of the Experiment - part 1 of 2
- Page 02 - Explanation of the Experiment - part 2 of 2
- Page 03 - Purpose of the Experiment and Parts Needed
- Page 04 - Do the Experiment (part 1 of 2)
- Page 05 - Do the Experiment (part 2 of 2)
- Page 06 - Crossword Puzzle
- Page 07 - Word Search Puzzle
- Page 08 - Written 10-Question Multiple Choice Quiz
- Page 09 - Answers to Crossword
- Page 10- Answers to Word Search
- Page 11 - Answer Key to Written Quiz
- Page 12 - Poster to put up on classroom wall
- Page 13 - Price List for Parts Kits for your to order more. Send Purchase Order to [Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com) or order online at [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)

Experiment Parts Kit  
**#MC1-00-PK**  
**Solderless Circuit Board**  
 Exciting, Educational and Fun



Experiment Parts only (packaged in a 3x5 inch resealable plastic bag.)  
**LEARN more today, EARN more tomorrow!**  
Copyright © Mr Circuit Technology 2024

For more info: [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)  
[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)

Science/Electronics Kits and Labs



Experiment Parts Kit  
**#MC1-18-PK**  
**"Variable Speed Lights Circuit"**  
 Exciting, Educational and Fun



Experiment Parts only (packaged in a 3x5 inch resealable plastic bag.)  
**LEARN more today, EARN more tomorrow!**  
Copyright © Mr Circuit Technology 2024

For more info: [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)  
[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)

Science/Electronics Kits and Labs

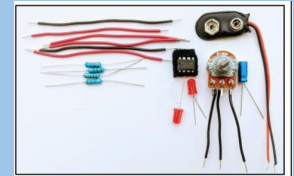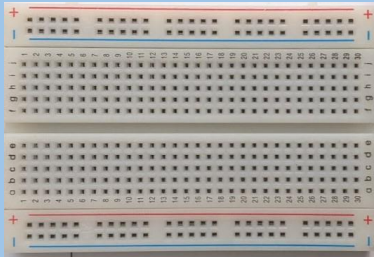

**PREPARATION:** You can put the Page 12 poster up on your classroom wall to announce the fact that you are going to do the Science-Electronics Experiment.

**Step 1** - Make a copy of pages 1 through 8 for each student. The students can read and do these pages on their own or you can guide them.

**Step 2** - Hand out Parts Kit #MC1-00-PK (that has the Solderless Circuit Board) and Parts Kit #MC1-18-PK (that has the experiment parts) with a 9-Volt battery. Give these items to each student along with the 8 pages.

**Step 3** - When your students have completed the experiment, collect all the Parts Kits and batteries for later use.

**Step 4** - Collect all the Written Quizzes for grading and use the Answer Key to grade them.


For Tech Support or any questions, you can email us or call 805-295-1642

Copyright © Mr Circuit Technology 2024



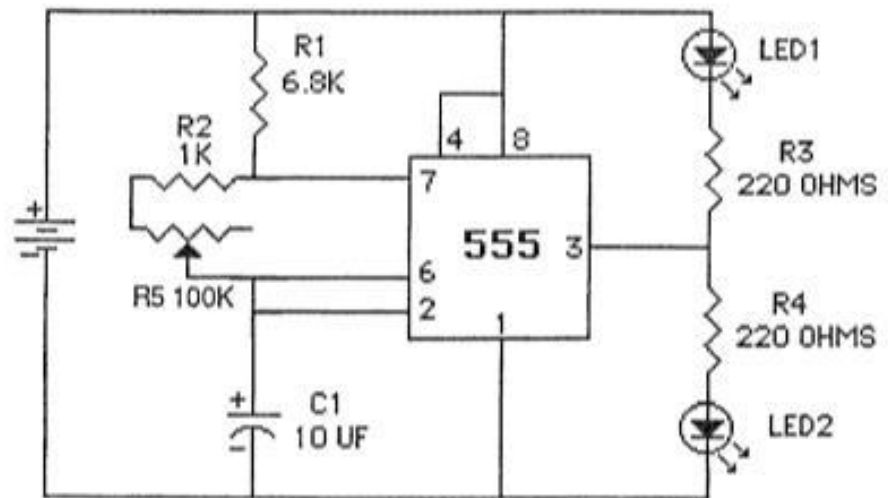**EXPLANATION OF EXPERIMENT part 1 of 2**

\*\*\* You are going to build a VARIABLE SPEED LIGHTS circuit. Here is the SCHEMATIC DIAGRAM of the circuit you will build.



This interesting circuit was invented by engineers who needed a circuit that would make lights blink alternately at a variable rate like disco lights.


This circuit has two LEDs that turn on and off alternately which makes an interesting light display.

You can use this circuit for a variety of purposes including burglar alarms, etc.

**(Continue to Page 2)**
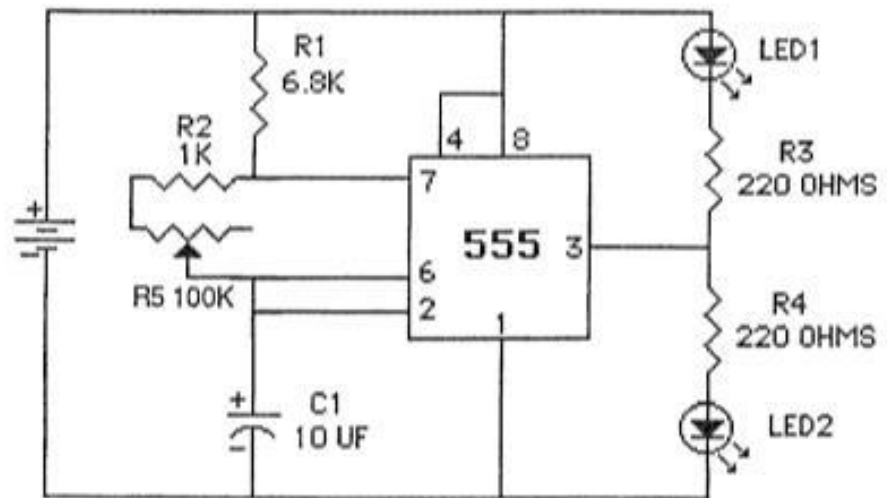
## EXPLANATION OF EXPERIMENT part 2 of 2

Let's talk about how the circuit works. Here is the schematic of the **VARIABLE SPEED LIGHTS** circuit that you will build.



The 555 IC in this circuit is working as a **CLOCK** which means the 555 is putting out clock pulses. The speed can be **adjusted** by rotating the shaft of the potentiometer.

The two LEDs are connected with **opposite polarity** to Pin 3. When Pin 3 is positive, electrons will leave the battery and flow through LED2 to Pin 3. When Pin 3 is negative, electrons will leave Pin 3 and go through LED1 and flow to the positive terminal of the battery.

**Note:** When the Anode of an LED is connected the Positive and the Cathode is connected to the negative, then the LED is Forward-Biased and the LED will light up. If the LED is Reverse-Biased, it will not light up.

**(Continue to Page 3)**

PURPOSE OF THIS EXPERIMENT

MC1-18-R-3

\*\*\* To build a VARIABLE SPEED LIGHTS circuit using a 555 Integrated circuit.

PARTS NEEDED FOR EXPERIMENT


In this experiment, you will use the following:



9-Volt Snap




555 IC

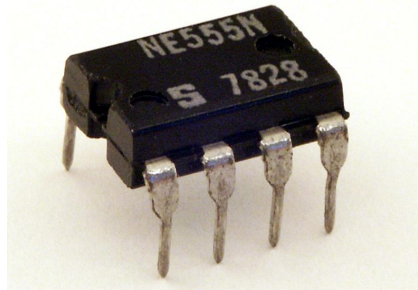

2 LEDs



Potentiometer

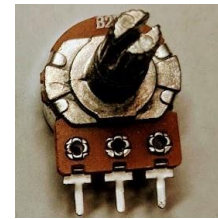


4 fixed Resistors



6 Jumper Wires




Solderless Circuit Board

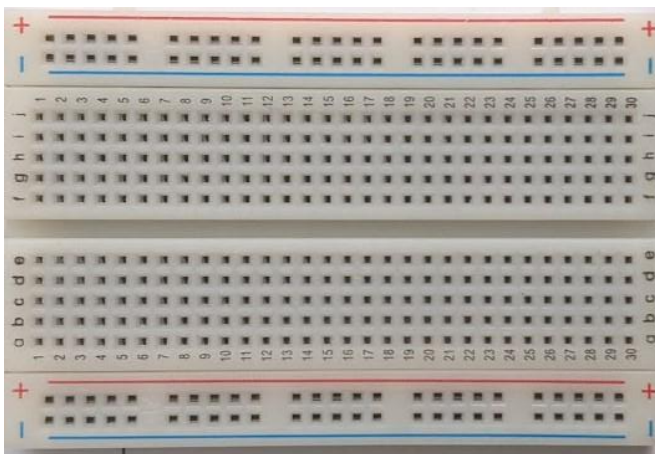

9-V Battery



Radial Capacitor

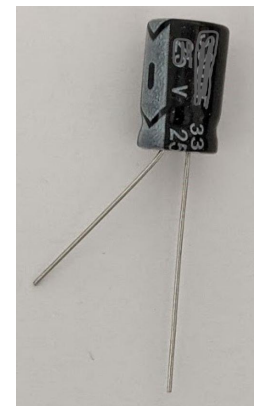

(Continue to Page 4)




## DO THE EXPERIMENT (part 1 of 2)

MC1-18-R-4

Now you are going to build the circuit on a Solderless CB.

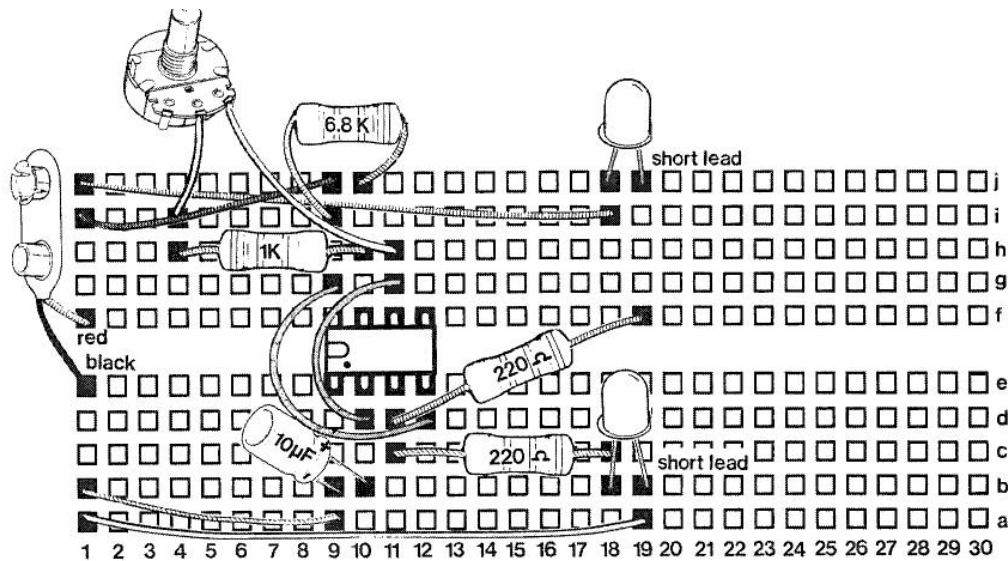Step 1 - Take out all the parts needed for this experiment.



Step 2 - Install all the parts on the SCB as shown above.


- Install an LED with the Short Lead in hole 19j and the Long Lead in hole 18j
- Install an LED with the Short Lead in hole 19b and the Long Lead in hole 18b
- Install the 220 Ohm resistor (red, red, brown, gold) in holes 11c to 18c
- Install the 220 Ohm resistor (red, red, brown, gold) in holes 11d to 19f
- Install the 6800 (6.8k) Ohm resistor (blue, gray, red, gold) in holes 9i to 10j
- Install the 555 Timer IC with Pin 1 in hole 9e as shown in pictorial
- Install the 10uF Electrolytic Capacitor - Long lead in hole 10b, Short lead in 9b
- Install the Potentiometer, middle lead in 4i, edge in 11h
- Install Jumper Wire #1 in holes 1a to 19a
- Install Jumper Wire #2 in holes 1b to 9a
- Install Jumper Wire #3 in holes 1i to 9j
- Install Jumper Wire #4 in holes 1j to 18i
- Install Jumper Wire #5 in holes 9g to 12d
- Install Jumper Wire #6 in holes 10d to 11g
- Install the Battery Snap, Black lead in hole 1e and Red Lead in hole 1f



(Continue to Page 5)

## DO THE EXPERIMENT (part 2 of 2)

MC1-18-R-5

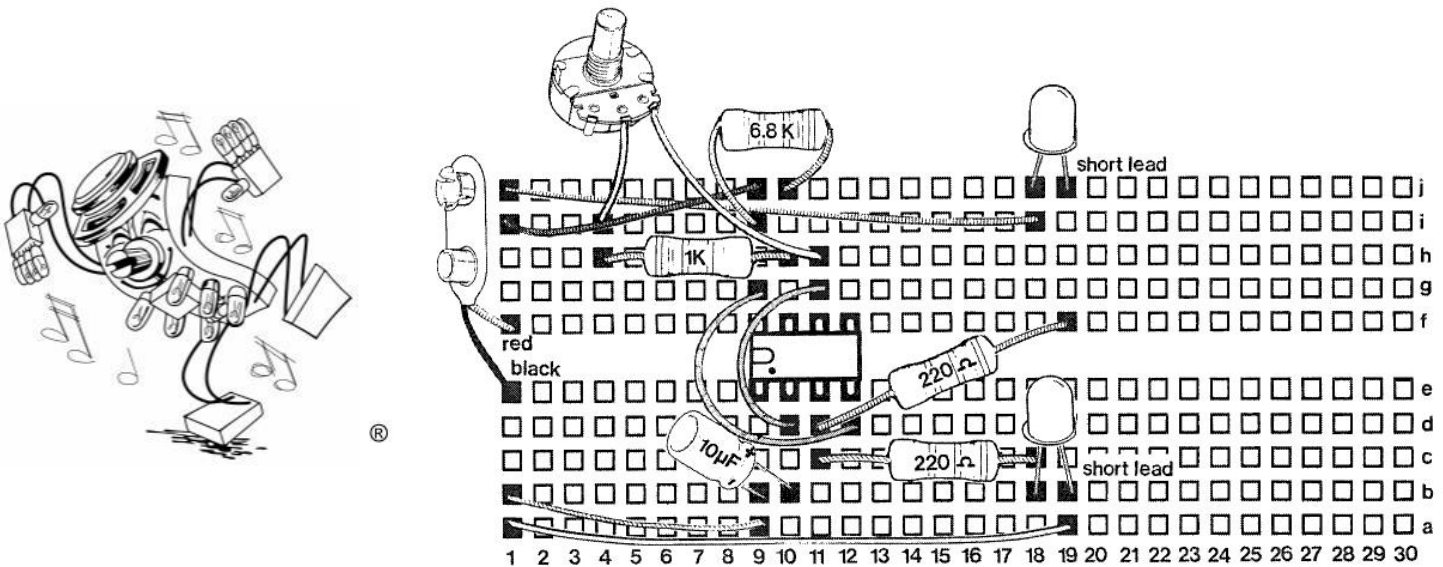

Step 3 - Connect the battery to the Battery Snap. The LEDs should blink on and off and you can vary the rate of blinking by twisting the shaft of the potentiometer.


## CONCLUSION

You should have observed that you can build a  
**VARIABLE SPEED LIGHTS** circuit  
 with a  
 555 Integrated Circuit.

**(End of Experiment 11)**

# CROSSWORD
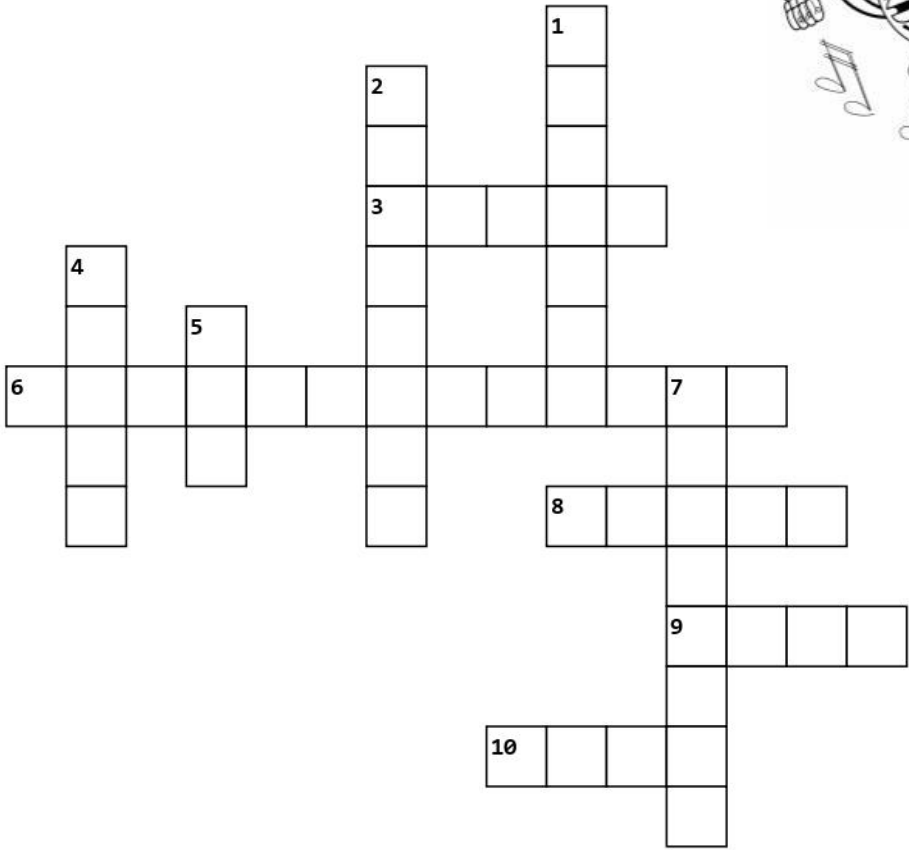
## Exp. 18 - "VARIABLE SPEED LIGHTS CIRCUIT"



**Across**

- 3.** This circuit produces an interesting \_\_\_\_\_ light display.
- 6.** We use a \_\_\_\_\_ to adjust the blinking rate.
- 8.** The 555 Integrated Circuit has \_\_\_\_\_ pins.
- 9.** How many volts does it take to power this circuit?
- 10.** What is the color of the first band on the 6.8k Ohm resistor?

**Down**

- 1.** The short lead on an LED is the \_\_\_\_\_ lead of the LED.
- 2.** The LEDs in this circuit are connected in opposite \_\_\_\_\_ .
- 4.** The 555 Integrated Circuit puts out \_\_\_\_\_ pulses.
- 5.** What is the color of the first band on the 220 Ohm resistor?
- 7.** The person who designed this circuit is called an \_\_\_\_\_ .

Exp. 18 - "VARIABLE SPEED LIGHTS CIRCUIT"

M A L T E R N A T E L Y K M D K J R D L  
Z K C F O Z L G O Q W L F W K Q X U Q R  
Z M R B P O T E N T I O M E T E R F V B  
X E A T D R S F P O S I T I V E A P Y I  
J F N D E S L S T F O T M O D V E L O K  
O M O B S X D F E L K E G Z I H X N K A  
R D D O D M T W N E G A T I V E I I K R  
K X E T R M E U F T H H O Y A J Y N B Q  
W T O K B D B C I Q G O U G M P Y E F B  
V M O R R B D F W H K U O T V S A V H E  
G R A K S K G F T X T Q J Z E W J E V B  
K T W U D G S N J O F Z M Y M L N G D J  
F G I X K H H E C P V K D W C J O C X X  
G V V C A E F A Z U T W F I M N C X Z N  
F N O E U K N H X L D A Y O N U I Q P H  
P L I Y Q V U X B S D I J M G J V R D S  
C T H R E E R N S E R X U Y L C H A F N  
Y Y B V E P L Z H S J F C L A L S B N O  
M K N N Z R S O I N K Q E D O H T A C J  
U V G M L K Y N J L W T V V P L R I U S



1. The 555 is working as a variable speed \_\_\_\_\_ in this circuit.
2. This component is used to vary the speed of the blinking LEDs.
3. The long lead on an LED is the \_\_\_\_\_ lead.
4. The short lead on an LED is the \_\_\_\_\_ lead.
5. It take this amount of volts to run this circuit.
6. The 555 Integrated circuit puts out clock \_\_\_\_\_ .
7. The \_\_\_\_\_ of the battery is connected to Pin 1 of the 555 Integrated Circuit.
8. The \_\_\_\_\_ of the battery is connected to Pins 4 and 8 of the 555 Integrated Circuit.
9. There are two 220 Ohm resistors connected to Pin \_\_\_\_\_ of the 555 IC.
10. The LEDs in this circuit blink \_\_\_\_\_ .





# QUIZ for Exp 18 or STEM KIT #18 in the Mr Circuit Electronics Training Lab 1

# (Page 8)



This Quiz covers the training learned by completing

## “Build a Variable Speed Lights Circuit” Experiment 18

Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A #1 This circuit uses \_\_\_\_\_  
working as a clock.

- B A. an NPN Transistor
- C B. a PNP Transistor
- D C. a 555 Timer IC
- A D. a Potentiometer

A #6 LED 1 is connect to pin 3 of the 555 Timer IC  
through \_\_\_\_\_ .

- B A. a 220 Ohm resistor
- C B. a 10uF capacitor
- D C. a 6.8k Ohm resistor
- A D. a 1k Ohm resistor

A #2 You can adjust the speed of the blinking  
lights by using \_\_\_\_\_ .

- B A. the Diode
- C B. the LED
- D C. the Potentiometer
- A D. the transistor

A #7 When this circuit is working, the LEDs will  
\_\_\_\_\_ .

- B A. remain on
- C B. remain off permanently
- D C. blink on and off alternately
- A D. get hot and self-destruct

A #3 The two LEDs in this circuit are installed in  
\_\_\_\_\_ polarity.

- B A. the same
- C B. amplifying
- D C. dual
- A D. opposite

A #8 When an LED is \_\_\_\_\_ it  
means that the Anode is positive and the  
Cathode is negative.

- B A. reverse-biased
- C B. will not turn on
- D C. forward biased
- A D. will change from Red to Green

A #4 What is the value of the capacitor connected  
to Pin 2 of the 555 Timer IC in this circuit?

- B A. 1000uF
- C B. 330uF
- D C. 33uF
- A D. 10uF

A #9 When an LED is \_\_\_\_\_ it  
means that the Anode is negative and the  
Cathode is positive.

- B A. will change from Red to Green
- C B. forward-biased
- D C. will not turn on
- A D. reverse-biased

A #5 If we reverse the polarity of the battery snap  
on the circuit, what will happen?

- B A. it will work just fine
- C B. the LED will burn out
- D C. you might destroy the 555 Timer IC
- A D. the LED will self-destruct


A #10 A Potentiometer is also known as  
\_\_\_\_\_ .

- B A. variable transistor
- C B. fixed capacitor
- D C. a variable resistor
- A D. fixed resistor

Score	
-------	--

**ANSWERS FOR CROSSWORD**

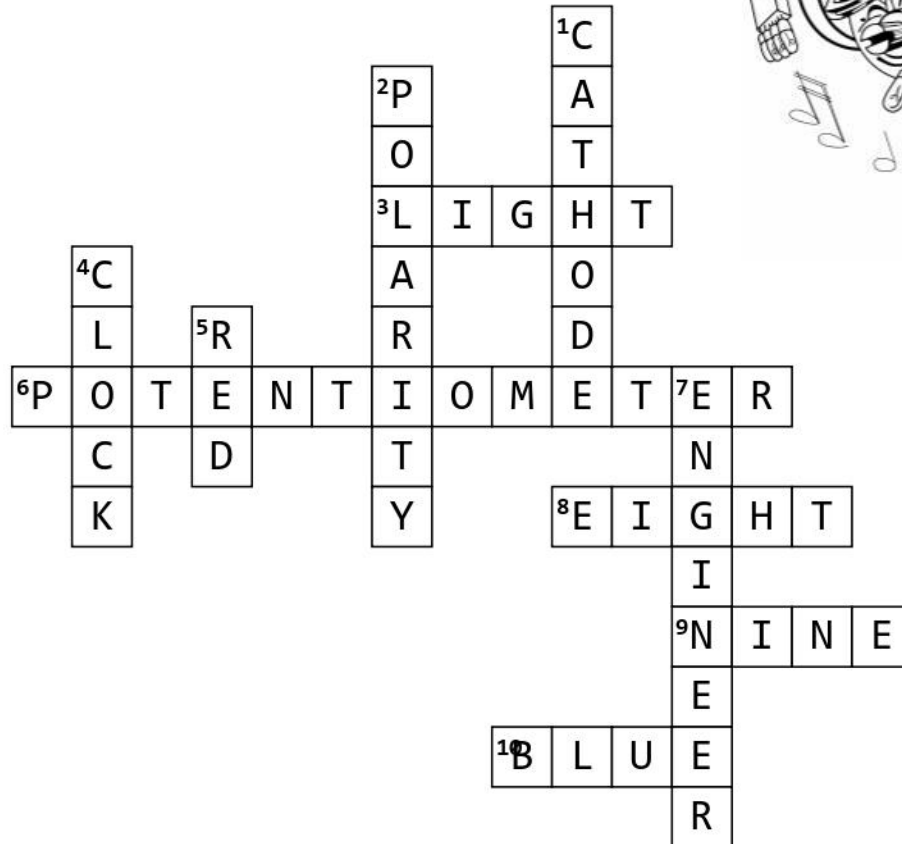**Exp. 18 - "VARIABLE SPEED LIGHTS CIRCUIT"**



**Across**

- 3. This circuit produces an interesting \_\_\_\_\_ light display.
- 6. We use a \_\_\_\_\_ to adjust the blinking rate.
- 8. The 555 Integrated Circuit has \_\_\_\_\_ pins.
- 9. How many volts does it take to power this circuit?
- 10. What is the color of the first band on the 6.8k Ohm resistor?

**Down**

- 1. The short lead on an LED is the \_\_\_\_\_ lead of the LED.
- 2. The LEDs in this circuit are connected in opposite \_\_\_\_\_.
- 4. The 555 Integrated Circuit puts out \_\_\_\_\_ pulses.
- 5. What is the color of the first band on the 220 Ohm resistor?
- 7. The person who designed this circuit is called an \_\_\_\_\_.

# ANSWERS FOR WORD SEARCH

## Exp. 18 - "VARIABLE SPEED LIGHTS CIRCUIT"

M A L T E R N A T E L Y K M D K J R D L  
 Z K C F O Z L G O Q W L F W K Q X U Q R  
 Z M R B P O T E N T I O M E T E R F V B  
 X E A T D R S F P O S I T I V E A P Y I  
 J F N D E S L S T F O T M O D V E L O K  
 O M O B S X D F E L K E G Z I H X N K A  
 R D D O D M T W N E G A T I V E I I K R  
 K X E T R M E U F T H H O Y A J Y N B Q  
 W T O K B D B C I Q G O U G M P Y E F B  
 V M O R R B D F W H K U O T V S A V H E  
 G R A K S K G F T X T Q J Z E W J E V B  
 K T W U D G S N J O F Z M Y M L N G D J  
 F G I X K H H E C P V K D W C J O C X X  
 G V V C A E F A Z U T W F I M N C X Z N  
 F N O E U K N H X L D A Y O N U I Q P H  
 P L I Y Q V U X B S D I J M G J V R D S  
C T H R E E R N S E R X U Y L C H A F N  
 Y Y B V E P L Z H S J F C L A L S B N O  
 M K N N Z R S O I N K Q E D O H T A C J  
 U V G M L K Y N J L W T V V P L R I U S



1. The 555 is working as a variable speed \_\_\_\_\_ in this circuit.
2. This component is used to vary the speed of the blinking LEDs.
3. The long lead on an LED is the \_\_\_\_\_ lead.
4. The short lead on an LED is the \_\_\_\_\_ lead.
5. It take this amount of volts to run this circuit.
6. The 555 Integrated circuit puts out clock \_\_\_\_\_ .
7. The \_\_\_\_\_ of the battery is connected to Pin 1 of the 555 Integrated Circuit.
8. The \_\_\_\_\_ of the battery is connected to Pins 4 and 8 of the 555 Integrated Circuit.
9. There are two 220 Ohm resistors connected to Pin \_\_\_\_\_ of the 555 IC.
10. The LEDs in this circuit blink \_\_\_\_\_ .

**QUICK-CHECK ANSWER KEY for Experiment 18 QUIZ  
for Mr Circuit Electronics Training (“Variable Speed Lights”)**

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

Count the right answers and record the score of right answers in your grade book.




<p>A B <b>C</b> D</p>	<p><b>#1</b> This circuit uses _____ working as a clock.</p> <p>A. an NPN Transistor B. a PNP Transistor C. a 555 Timer IC D. a Potentiometer</p>	<p><b>#6</b> LED 1 is connect to pin 3 of the 555 Timer IC through _____ .</p> <p>A. a 220 Ohm resistor B. a 10uF capacitor C. a 6.8k Ohm resistor D. a 1k Ohm resistor</p>	<p><b>A</b> B C D</p>
<p>A B <b>C</b> D</p>	<p><b>#2</b> You can adjust the speed of the blinking lights by using _____ .</p> <p>A. the Diode B. the LED C. the Potentiometer D. the transistor</p>	<p><b>#7</b> When this circuit is working, the LEDs will _____ .</p> <p>A. remain on B. remain off permanently C. blink on and off alternately D. get hot and self-destruct</p>	<p>A B <b>C</b> D</p>
<p>A B C <b>D</b></p>	<p><b>#3</b> The two LEDs in this circuit are installed in _____ polarity.</p> <p>A. the same B. amplifying C. dual D. opposite</p>	<p><b>#8</b> When an LED is _____ it means that the Anode is positive and the Cathode is negative.</p> <p>A. reverse-biased B. will not turn on C. forward biased D. will change from Red to Green</p>	<p>A B <b>C</b> D</p>
<p>A B C <b>D</b></p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?</p> <p>A. 1000uF B. 330uF C. 33uF D. 10uF</p>	<p><b>#9</b> When an LED is _____ it means that the Anode is negative and the Cathode is positive.</p> <p>A. will change from Red to Green B. forward-biased C. will not turn on D. reverse-biased</p>	<p>A B C <b>D</b></p>
<p>A B <b>C</b> D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p>A. it will work just fine B. the LED will burn out C. you might destroy the 555 Timer IC D. the LED will self-destruct</p>	<p><b>#10</b> A Potentiometer is also known as _____ .</p> <p>A. variable transistor B. fixed capacitor C. a variable resistor D. fixed resistor</p>	<p>A B <b>C</b> D</p>



# **BUILD A BETTER FUTURE by UNDERSTANDING SCIENCE-ELECTRONICS**

## **VARIABLE SPEED LIGHTS**


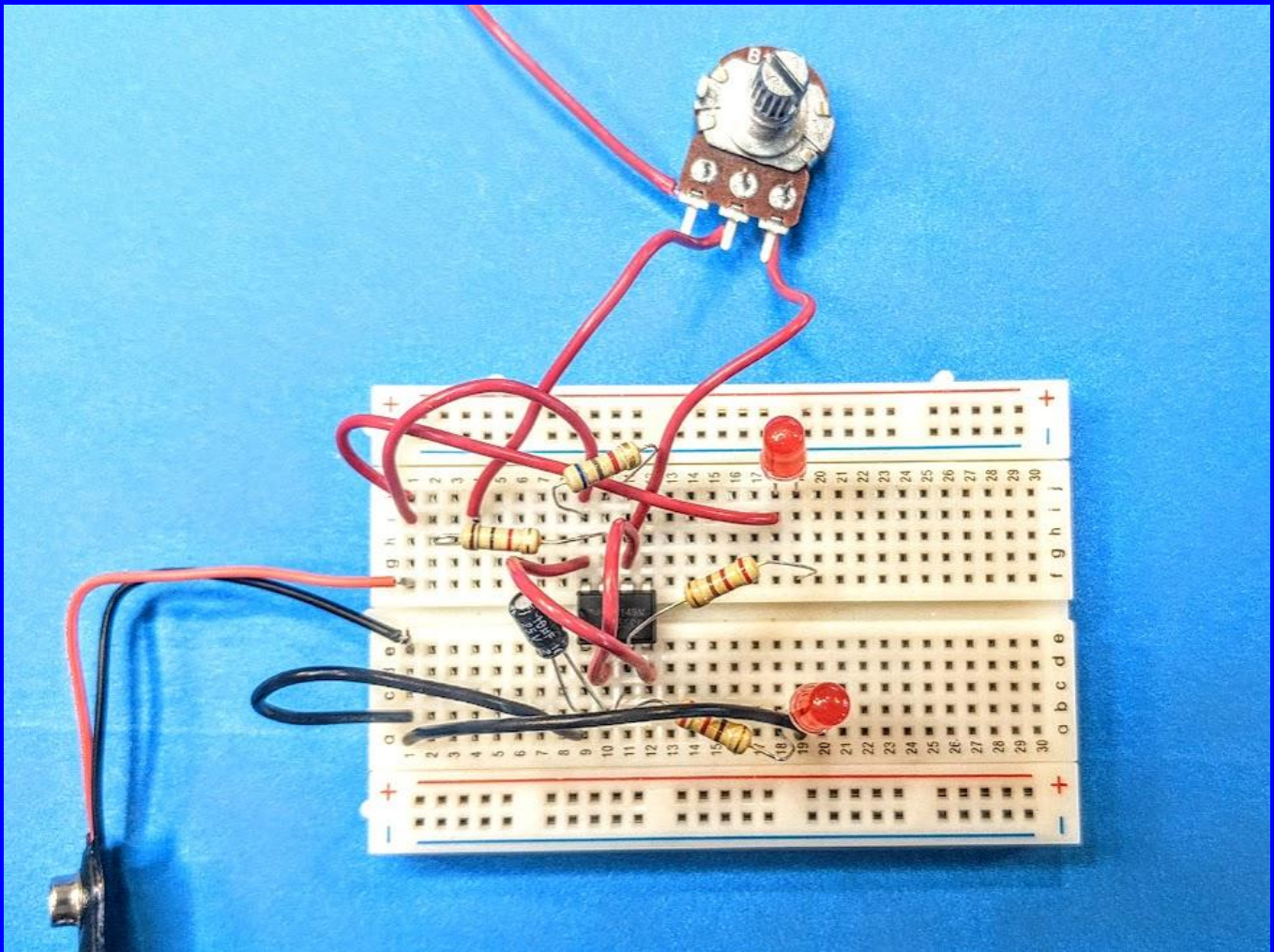


**BASIC ELECTRONICS LAB 1**

## **“VARIABLE SPEED LIGHTS CIRCUIT”**

**(Poster MC1-18-P01)**

**(Page 12)**

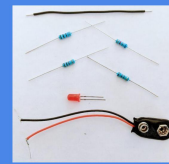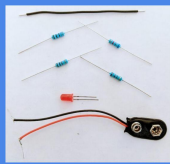

## PRICE LIST

PARTS KIT	Mr Circuit Series 1	Price
Number	PARTS KITS FOR "LESSON PLANS"	Each
MC1-00-PK	Solderless Circuit Board to build kits	\$3.95
MC1-01-PK	Parts Kit for "How a Resistor Works	\$1.95
MC1-02-PK	Parts Kit for "How a Potentiometer Works	\$2.95
MC1-03-PK	Parts Kit for "How a Photocell Works	\$1.95
MC1-04-PK	Parts Kit for "How a Capacitor Works	\$2.95
MC1-05-PK	Parts Kit for "How a Speaker Works	\$2.95
MC1-06-PK	Parts Kit for "How a Diode Works	\$1.95
MC1-07-PK	Parts Kit for "How an SCR Works	\$3.95
MC1-08-PK	Parts Kit for "How an NPN Transistor Works	\$2.95
MC1-09-PK	Parts Kit for "How a PNP Transistor Works	\$2.95
MC1-10-PK	Parts Kit for "How a Transistor Oscillator Works	\$3.95
MC1-11-PK	Parts Kit for "How a 555 Timer IC Works	\$2.95
MC1-12-PK	Parts Kit for "Burglar Alarm circuit	\$3.95
MC1-13-PK	Parts Kit for "Solar-Activated Night Light circuit	\$3.95
MC1-14-PK	Parts Kit for "0 TO 9V DC Power Supply circuit	\$2.95
MC1-15-PK	Parts Kit for "Electronic Metronome circuit	\$4.95
MC1-16-PK	Parts Kit for "Electronic Motorcycle circuit	\$3.95
MC1-17-PK	Parts Kit for "Railroad Lights circuit	\$2.95
MC1-18-PK	Parts Kit for "Variable Speed Lights circuit	\$3.95
MC1-19-PK	Parts Kit for "Continuity Tester circuit	\$4.95
MC1-20-PK	Parts Kit for "Audio Generator circuit	\$5.95
MC1-21-PK	Parts Kit for "Electronic Police Siren circuit	\$4.95
MC1-22-PK	Parts Kit for "Solar-Activated Wake-Up Alarm circuit	\$3.95
MC1-23-PK	Parts Kit for "Variable Timer circuit	\$3.95
MC1-24-PK	Parts Kit for "Moisture Detector circuit	\$2.95
MC1-25-PK	Parts Kit for "Code Oscillator circuit	\$4.95
MC1-26-PK	Parts Kit for "Audible Water Detector circuit	\$4.95
MC1-27-PK	Parts Kit for "English Police Siren circuit	\$4.95
MC1-28-PK	Parts Kit for "Electronic Canary circuit	\$7.95
MC1-29-PK	Parts Kit for "fantasy Space Machine Gun circuit	\$5.95
MC1-30-PK	Parts Kit for "Ultrasonic Pest Repeller circuit	\$5.95
<b>MC1-SET-PK</b>	<b>Complete Set of All Series 1 Parts Kits (31 total)</b>	<b>\$120.00</b>