

For more info:

[www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)

[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)

# Mr Circuit Technology

Science/Electronics Experiment Kits and Labs


## Exp. 19 - "CONTINUITY TESTER CIRCUIT"

### LESSON PLAN

#### Table of Contents

- Page 01 - Explanation of the Experiment - part 1 of 2
- Page 02 - Explanation of the Experiment - part 2 of 2
- Page 03 - Purpose of the Experiment and Parts Needed
- Page 04 - Do the Experiment (part 1 of 2)
- Page 05 - Do the Experiment (part 2 of 2)
- Page 06 - Crossword Puzzle
- Page 07 - Word Search Puzzle
- Page 08 - Written 10-Question Multiple Choice Quiz
- Page 09 - Answers to Crossword
- Page 10- Answers to Word Search
- Page 11 - Answer Key to Written Quiz
- Page 12 - Poster to put up on classroom wall
- Page 13 - Price List for Parts Kits for your to order more. Send Purchase Order to [Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com) or order online at [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)

Experiment Parts Kit  
**#MC1-00-PK**  
**Solderless Circuit Board**  
 Exciting, Educational and Fun



Experiment Parts only (packaged in a 3x5 inch resealable plastic bag.)  
**LEARN more today, EARN more tomorrow!**  
Copyright © Mr Circuit Technology 2024



For more info: [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)  
[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)  
 Science/Electronics Kits and Labs

Experiment Parts Kit  
**#MC1-19-PK**  
**"Continuity Tester Circuit"**  
 Exciting, Educational and Fun



Experiment Parts only (packaged in a 3x5 inch resealable plastic bag.)  
**LEARN more today, EARN more tomorrow!**  
Copyright © Mr Circuit Technology 2024

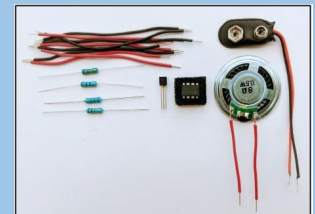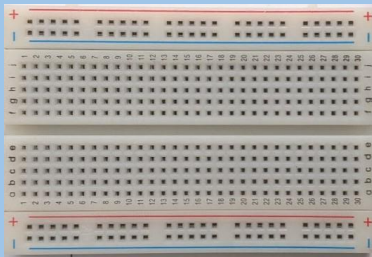For more info: [www.MrCircuitTechnology.com](http://www.MrCircuitTechnology.com)  
[Gary@MrCircuitTechnology.com](mailto:Gary@MrCircuitTechnology.com)  
 Science/Electronics Kits and Labs



**PREPARATION:** You can put the Page 12 poster up on your classroom wall to announce the fact that you are going to do the Science-Electronics Experiment.

**Step 1** - Make a copy of pages 1 through 8 for each student. The students can read and do these pages on their own or you can guide them.

**Step 2** - Hand out Parts Kit #MC1-00-PK (that has the Solderless Circuit Board) and Parts Kit #MC1-19-PK (that has the experiment parts) with a 9-Volt battery. Give these items to each student along with the 8 pages.

**Step 3** - When your students have completed the experiment, collect all the Parts Kits and batteries for later use.



**Step 4** - Collect all the Written Quizzes for grading and use the Answer Key to grade them.



For Tech Support or any questions, you can email us or call 805-295-1642

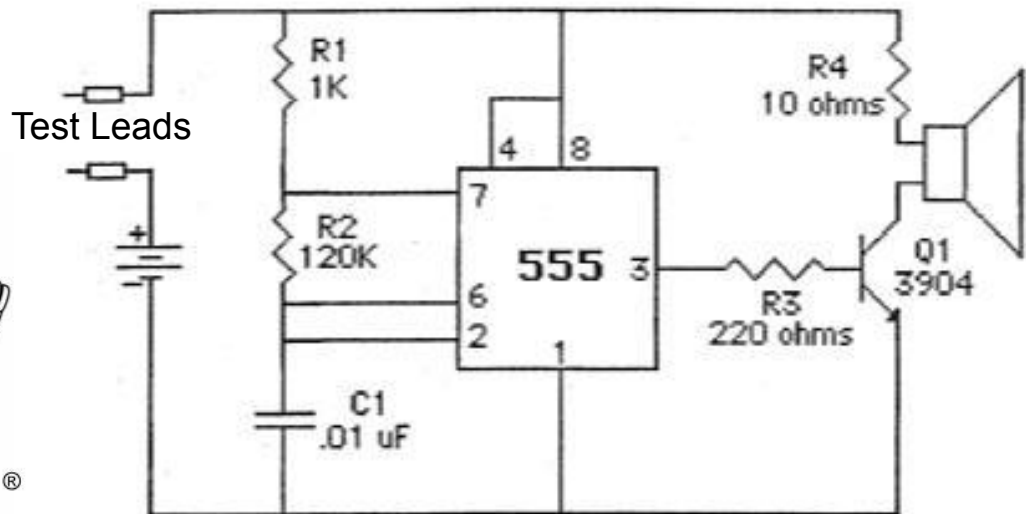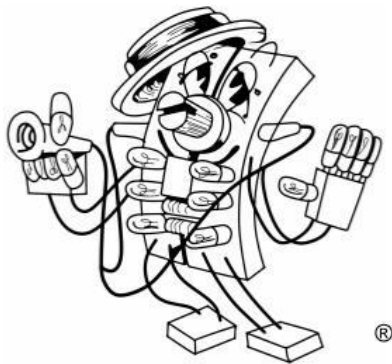**EXPLANATION OF EXPERIMENT part 1 of 2**

\*\*\* You are going to build a CONTINUITY TESTER circuit. Here is the SCHEMATIC DIAGRAM of the circuit you will build.



This interesting circuit was invented by engineers who needed a circuit that a technician could use to check for electrical continuity.

With his continuity tester you can check incandescent light bulbs, fuses, and circuits for continuity.


(Note: You cannot use this circuit to test LEDs. LEDs do not have a filament which is a thin wire that emits light in an incandescent light bulb. With time, this thin wire breaks in a light bulb so this checker will work on incandescent light bulbs.)

Touch the Test Leads to either end of a fuse and if you hear a tone, the fuse is good.

**(Continue to Page 2)**

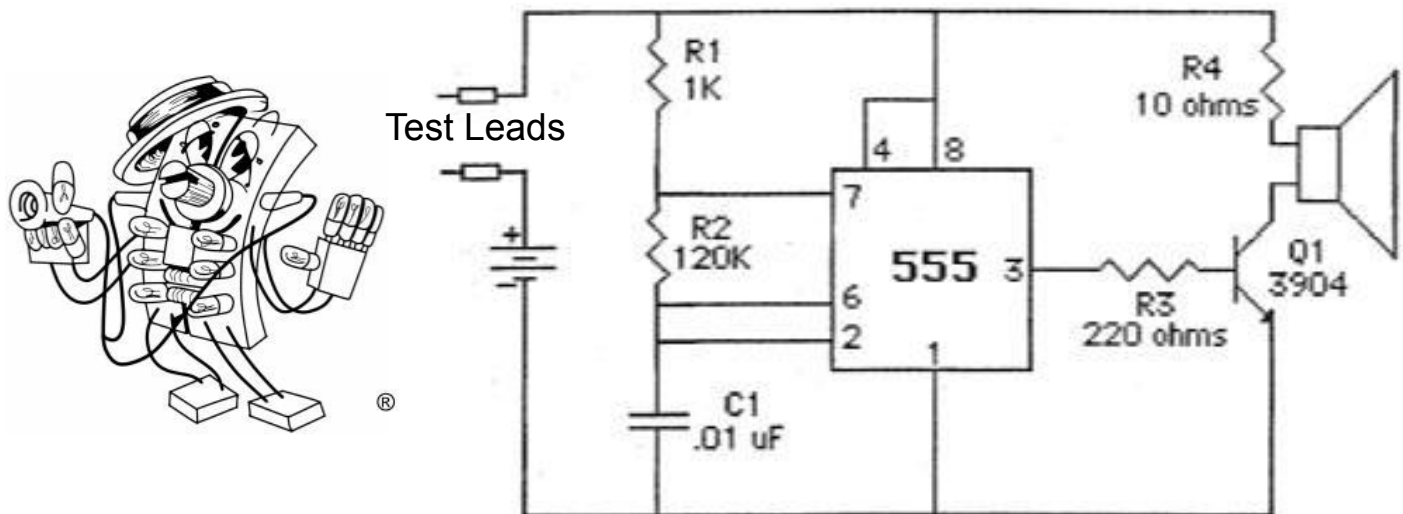**EXPLANATION OF EXPERIMENT part 2 of 2**

Let's talk about how the circuit works. Here is the schematic of the **CONTINUITY TESTER** circuit that you will build.



The 555 IC in this circuit is working as a **CLOCK** which means the 555 is putting out clock pulses.

The pulses coming from Pin 3 on the 555 are sent to the speaker through a transistor. The transistor amplifies the sound and makes it louder.

When the Test Leads sense continuity, the circuit is completed and there is a tone emitted from the speaker.

This is a great addition to any technicians tool box for troubleshooting electronics.

**(Continue to Page 3)**

**PURPOSE OF THIS EXPERIMENT**

\*\*\* To build a CONTINUITY TESTER circuit using a 555 Integrated circuit.

MC1-19-R-3




**PARTS NEEDED FOR EXPERIMENT**

In this experiment, you will use the following:


**9-Volt Snap**



**555 IC**

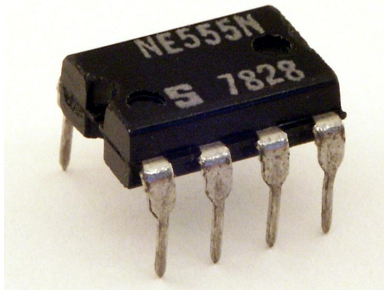

**NPN**

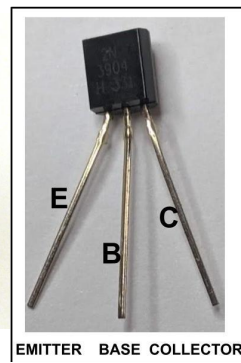

**Speaker**




**4 fixed Resistors**



**8 Jumper Wires**



**Solderless Circuit Board**

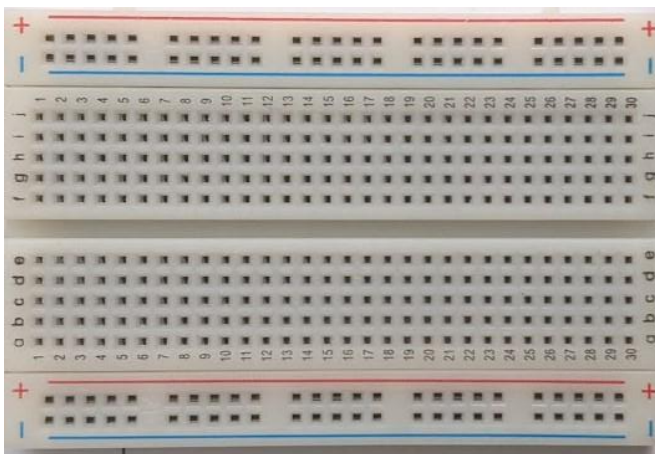

**9-V Battery**



**Disc Capacitor**



(Continue to Page 4)




## DO THE EXPERIMENT (part 1 of 2)

MC1-19-R-4

Now you are going to build the circuit on a Solderless CB.

Step 1 - Take out all the parts needed for this experiment.

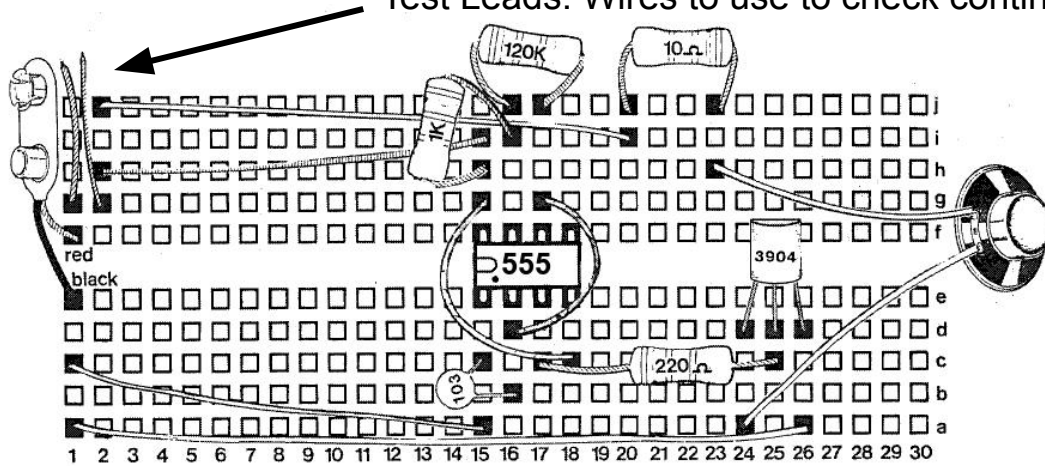Test Leads: Wires to use to check continuity



Step 2 - Install all the parts on the SCB as shown above.

- Install the 10 Ohm resistor (brown, black, black, gold) in holes 20j to 23j
- Install the 220 Ohm resistor (red, red, brown, gold) in holes 17c to 25c
- Install the 1000 (1k) Ohm resistor (brown, black, red, gold) in holes 15h to 16i
- Install the 120k Ohm resistor (brown, red, yellow, gold) in holes 16j to 17j
- Install the 555 Timer IC with Pin 1 in hole 15e as shown in pictorial
- Install one 0.01uF (103) disc Capacitor in holes 15c to 16b
- Install one NPN 3904 Transistor -Collector in 24d, Base in 25d, Emitter in 26d
- Install Jumper Wire #1 in holes 1a to 26a
- Install Jumper Wire #2 in holes 1c to 15a
- Install Jumper Wire #3 in holes 1g to loose end
- Install Jumper Wire #4 in holes 2g to loose end
- Install Jumper Wire #5 in holes 2j to 20i
- Install Jumper Wire #6 in holes 2h to 15i
- Install Jumper Wire #7 in holes 15g to 18c
- Install Jumper Wire #8 in holes 16d to 17g
- Install the Battery Snap, Black lead in hole 1e and Red Lead in hole 1f




(Continue to Page 5)
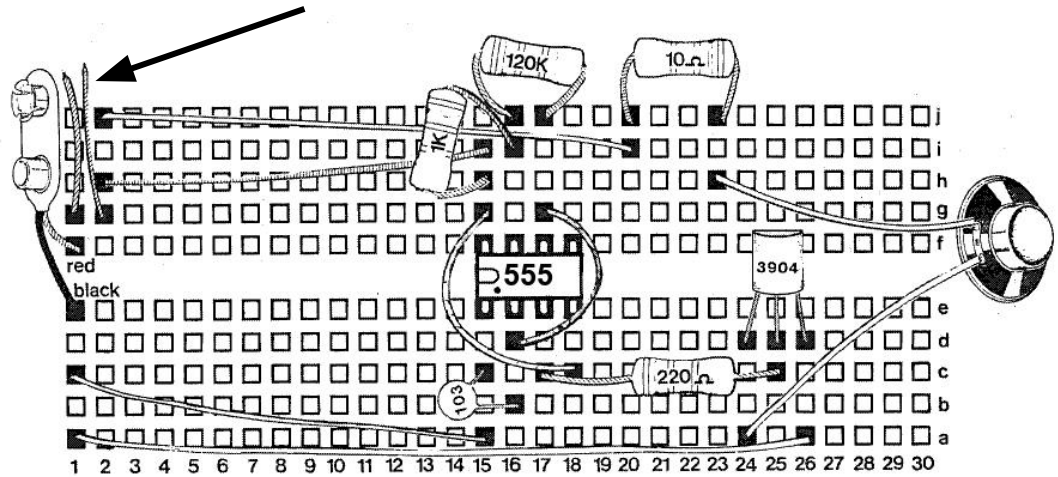
## DO THE EXPERIMENT (part 2 of 2)

MC1-19-R-5

Test Leads: Wires to use to check continuity



Step 3 - Connect the battery to the Battery Snap. The wires that are in holes 1g and 2g are used to check for continuity. Touch these wires to both ends of a fuse and if you hear a tone from the speaker, then the fuse is good.


## CONCLUSION

You should have observed that you can build a  
CONTINUITY CHECKER circuit  
with a  
555 Integrated Circuit.

**(End of Experiment 11)**

# CROSSWORD

## Exp. 19 - "CONTINUITY TESTER CIRCUIT"

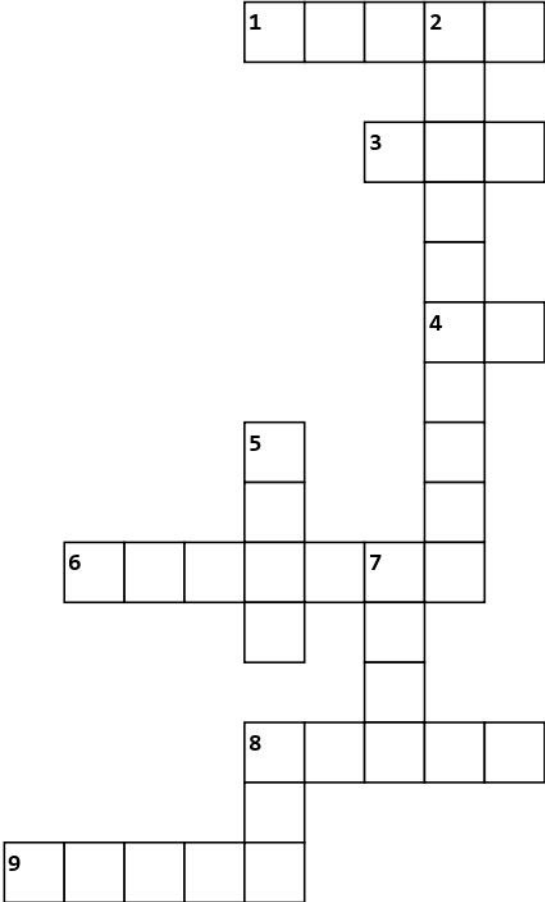

**Across**

- 1. The 555 in this circuit is working as a \_\_\_\_\_ .
- 3. How many capacitors does this circuit use?
- 4. Can this circuit be used to check LEDs?
- 6. The purpose of the transistor in this circuit is to \_\_\_\_\_ the loudness of the tone.
- 8. The tone in this circuit is emitted from Pin \_\_\_\_\_ of the 555 IC.
- 9. When there is continuity, the circuit will emit an \_\_\_\_\_ tone.

**Down**

- 2. When you check a fuse, you are checking for ELECTRICAL \_\_\_\_\_ .
- 5. You can use this circuit to test continuity in an incandescent light \_\_\_\_\_ .
- 7. How many fixed resistors are in this circuit?
- 8. How many probes are used to check for continuity?

**WORD SEARCH**

MC1-19-WS

**Exp. 19 - "CONTINUITY TESTER CIRCUIT"**



T D M M B R U W P Z Z S X M Z O X G S A  
 L V F V V U Y C N E T B B L P S W X D I  
 Q F P T U W D T P Q D P S C U R J R B X  
 B F P G Q M T E S B O M B M L N S A X B  
 T F Q E X E H S I M I B Y L S N S Z F E  
 U Y M K E B C T T Y S G A R E R L J V J  
 A T Y P C F P Q U P P I U U S B L M J Q  
 P F J W A M P N O X P H D D F N D Y Z N  
 T Z C B A Y I K C T P V I P A I E S R P  
 P B V K P C T U S B D T O I L Y Y H A I  
 E X J C A R T S N F V D B I T P C F L C  
 F N Q N O A V X J Z X E E T H R X A S T  
 D C U J S C H E M A T I C S K T I W Q O  
 C H X G X B Y V R C C I C V U C V M I R  
 T P L G P U K S P E W Z X W D F O F Q I  
 C D T Q Y L X L P R B U H Y T V Y L C A  
 Z P C U U B D Z W F Q M F E L L M D C L  
 F F K Q L O F H B A M P L I F Y L G L U  
 Z Q I O W Z Z J O U L R Q K G O Z O R Q  
 Y G J X V O L T S M F C W N F D B X P D

1. The diagram that shows the symbols for all the components in a circuit is called a \_\_\_\_\_.
2. The diagram that shows a drawing of all the parts on a solderless circuit board is called a \_\_\_\_\_.
3. This circuit is powered by nine \_\_\_\_\_.
4. The 555 IC in this circuit is used as a \_\_\_\_\_.
5. To check for continuity, use the two \_\_\_\_\_ LEADS.
6. The 555 IC generates an \_\_\_\_\_ signal.
7. The \_\_\_\_\_ from the 555 IC are sent to the transistor.
8. The transistor is used to \_\_\_\_\_ the audio signal.
9. You can use this circuit to test a \_\_\_\_\_.
10. You can use this to test an incandescent \_\_\_\_\_.






QUIZ for Exp 19 or STEM KIT #19 in the Mr Circuit Electronics Training Lab 1

This Quiz covers the training learned by completing

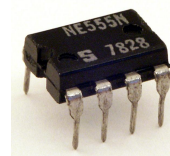“Build a Continuity Tester Circuit” Experiment 19



Circle the letter for your answer to each question and then hand this quiz in to your teacher.

A #1 This circuit uses 555 Timer IC working as a \_\_\_\_\_.

- B A. an amplifier
C B. a timer
D C. a clock
D D. a light generator

#6 Resistor R3 is connected to \_\_\_\_\_ of the 555 Timer IC.

- A. Pin 3
B. Pin 4
C. Pin 1
D. Pin 6

A #2 The loudness of the tone is \_\_\_\_\_.

- B A. adjustable
C B. fixed
D C. controlled by Resistor R1
D D. controlled by Capacitor C1

#7 When this circuit is working, the speaker will \_\_\_\_\_ when there is continuity.

- A. remain silent
B. self-destruct
C. emit a tone
D. get hot

A #3 The speaker in this circuit is connected to the \_\_\_\_\_ of transistor Q1.

- B A. Gate
C B. Emitter
D C. Collector
D D. Base

#8 When you touch the two probes together, the speaker will \_\_\_\_\_.

- A. remain silent
B. self-destruct
C. get hot
D. emit a tone

A #4 What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?

- B A. 0.01uF
C B. 330uF
D C. 33uF
D D. 10uF

#9 One probe is connected to R1 and the other one is connected \_\_\_\_\_.

- A. to the negative of the battery
B. to the speaker
C. to the 0.01uF capacitor
D. to the positive of the battery

A #5 If we reverse the polarity of the battery snap on the circuit, what will happen?

- B A. you might destroy the 555 Timer IC
C B. the LED will burn out
D C. it will work just fine
D D. the LED will self-destruct


#10 This circuit emits \_\_\_\_\_ signal.

- A. an inaudible
B. an rf
C. an ultrasonic
D. an audio

Score [ ]

**ANSWERS FOR CROSSWORD**

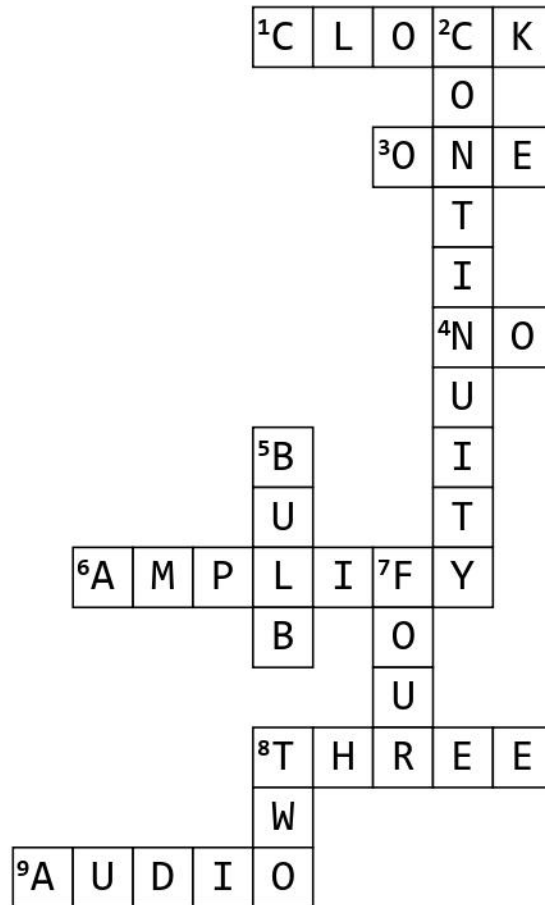**Exp. 19 - "CONTINUITY TESTER CIRCUIT"**



**Across**

1. The 555 in this circuit is working as a \_\_\_\_\_ .
3. How many capacitors does this circuit use?
4. Can this circuit be used to check LEDs?
6. The purpose of the transistor in this circuit is to \_\_\_\_\_ the loudness of the tone.
8. The tone in this circuit is emitted from Pin \_\_\_\_\_ of the 555 IC.
9. When there is continuity, the circuit will emit an \_\_\_\_\_ tone.

**Down**

2. When you check a fuse, you are checking for ELECTRICAL \_\_\_\_\_ .
5. You can use this circuit to test continuity in an incandescent light \_\_\_\_\_ .
7. How many fixed resistors are in this circuit?
8. How many probes are used to check for continuity?

# ANSWERS FOR WORD SEARCH

## Exp. 19 - "CONTINUITY TESTER CIRCUIT"


T D M M B R U W P Z Z S X M Z O X G S A  
 L V F V V U Y C N E T B B L P S W X D I  
 Q F P T U W D T P Q D P S C U R J R B X  
 B F P G Q M T E S B O M B M L N S A X B  
 T F Q E X E H S I M I B Y L S N S Z F E  
 U Y M K E B C T T Y S G A R E R L J V J  
 A T Y P C F P Q U P P I U U S B L M J Q  
 P F J W A M P N O X P H D D F N D Y Z N  
 T Z C B A Y I K C T P V I P A I E S R P  
 P B V K P C T U S B D T O I L Y Y H A I  
 E X J C A R T S N F V D B I T P C F L C  
 F N Q N O A V X J Z X E E T H R X A S T  
 D C U J S C H E M A T I C S K T I W Q O  
 C H X G X B Y V R C C I C V U C V M I R  
 T P L G P U K S P E W Z X W D F O F Q I  
 C D T Q Y L X L P R B U H Y T V Y L C A  
 Z P C U U B D Z W F Q M F E L L M D C L  
 F F K Q L O F H B A M P L I F Y L G L U  
 Z Q I O W Z Z J O U L R Q K G O Z O R Q  
 Y G J X V O L T S M F C W N F D B X P D

1. The diagram that shows the symbols for all the components in a circuit is called a \_\_\_\_\_.
2. The diagram that shows a drawing of all the parts on a solderless circuit board is called a \_\_\_\_\_.
3. This circuit is powered by nine \_\_\_\_\_.
4. The 555 IC in this circuit is used as a \_\_\_\_\_.
5. To check for continuity, use the two \_\_\_\_\_ LEADS.
6. The 555 IC generates an \_\_\_\_\_ signal.
7. The \_\_\_\_\_ from the 555 IC are sent to the transistor.
8. The transistor is used to \_\_\_\_\_ the audio signal.
9. You can use this circuit to test a \_\_\_\_\_.
10. You can use this to test an incandescent \_\_\_\_\_.

**QUICK-CHECK ANSWER KEY for Experiment 19 QUIZ  
for Mr Circuit Electronics Training (“Continuity Tester”)**

Place this sheet over top of the STUDENT QUIZ (offset a little to the left and then offset to the right) to compare the answers on this sheet to the answers that the student marked. Put an ‘X’ for each wrong answer.

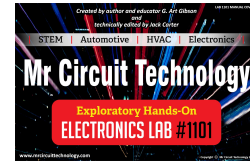Count the right answers and record the score of right answers in your grade book.




<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#1</b> This circuit uses 555 Timer IC working as a _____ .</p> <p><b>A.</b> an amplifier <b>B.</b> a timer <b>C.</b> a clock <b>D.</b> a light generator</p>	<p><b>#6</b> Resistor R3 is connected to _____ of the 555 Timer IC.</p> <p><b>A.</b> Pin 3 <b>B.</b> Pin 4 <b>C.</b> Pin 1 <b>D.</b> Pin 6</p>	<p>A</p> <p>B</p> <p>C</p> <p>D</p>
<p>A</p> <p><input checked="" type="radio"/> B</p> <p>C</p> <p>D</p>	<p><b>#2</b> The loudness of the tone is _____ .</p> <p><b>A.</b> adjustable <b>B.</b> fixed <b>C.</b> controlled by Resistor R1 <b>D.</b> controlled by Capacitor C1</p>	<p><b>#7</b> When this circuit is working, the speaker will _____ when there is continuity.</p> <p><b>A.</b> remain silent <b>B.</b> self-destruct <b>C.</b> emit a tone <b>D.</b> get hot</p>	<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>
<p>A</p> <p>B</p> <p><input checked="" type="radio"/> C</p> <p>D</p>	<p><b>#3</b> The speaker in this circuit is connected to the _____ of transistor Q1.</p> <p><b>A.</b> Gate <b>B.</b> Emitter <b>C.</b> Collector <b>D.</b> Base</p>	<p><b>#8</b> When you touch the two probes together, the speaker will _____ .</p> <p><b>A.</b> remain silent <b>B.</b> self-destruct <b>C.</b> get hot <b>D.</b> emit a tone</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#4</b> What is the value of the capacitor connected to Pin 2 of the 555 Timer IC in this circuit?</p> <p><b>A.</b> 0.01uF <b>B.</b> 330uF <b>C.</b> 33uF <b>D.</b> 10uF</p>	<p><b>#9</b> One probe is connected to R1 and the other one is connected _____ .</p> <p><b>A.</b> to the negative of the battery <b>B.</b> to the speaker <b>C.</b> to the 0.01uF capacitor <b>D.</b> to the positive of the battery</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>
<p><input checked="" type="radio"/> A</p> <p>B</p> <p>C</p> <p>D</p>	<p><b>#5</b> If we reverse the polarity of the battery snap on the circuit, what will happen?</p> <p><b>A.</b> you might destroy the 555 Timer IC <b>B.</b> the LED will burn out <b>C.</b> it will work just fine <b>D.</b> the LED will self-destruct</p>	<p><b>#10</b> This circuit emits _____ signal.</p> <p><b>A.</b> an inaudible <b>B.</b> an rf <b>C.</b> an ultrasonic <b>D.</b> an audio</p>	<p>A</p> <p>B</p> <p>C</p> <p><input checked="" type="radio"/> D</p>



# **BUILD A BETTER FUTURE by UNDERSTANDING SCIENCE-ELECTRONICS**

## **CONTINUITY TESTER**


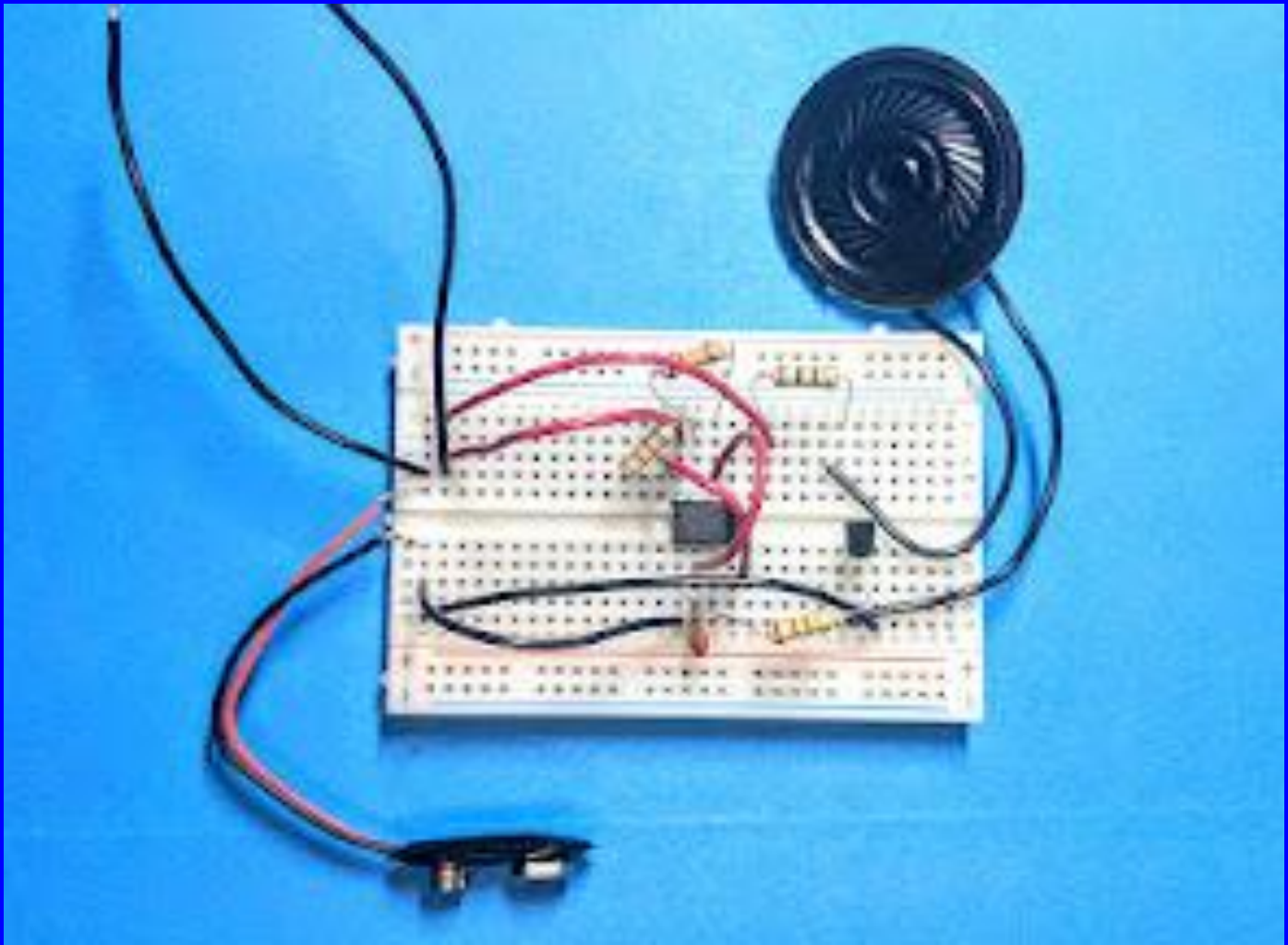


**BASIC ELECTRONICS LAB 1**

## **“CONTINUITY TESTER CIRCUIT”**

**(Poster MC1-19-P01)**

**(Page 12)**

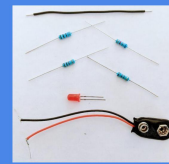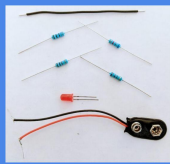

## PRICE LIST

PARTS KIT	Mr Circuit Series 1	Price
Number	PARTS KITS FOR "LESSON PLANS"	Each
MC1-00-PK	Solderless Circuit Board to build kits	\$3.95
MC1-01-PK	Parts Kit for "How a Resistor Works	\$1.95
MC1-02-PK	Parts Kit for "How a Potentiometer Works	\$2.95
MC1-03-PK	Parts Kit for "How a Photocell Works	\$1.95
MC1-04-PK	Parts Kit for "How a Capacitor Works	\$2.95
MC1-05-PK	Parts Kit for "How a Speaker Works	\$2.95
MC1-06-PK	Parts Kit for "How a Diode Works	\$1.95
MC1-07-PK	Parts Kit for "How an SCR Works	\$3.95
MC1-08-PK	Parts Kit for "How an NPN Transistor Works	\$2.95
MC1-09-PK	Parts Kit for "How a PNP Transistor Works	\$2.95
MC1-10-PK	Parts Kit for "How a Transistor Oscillator Works	\$3.95
MC1-11-PK	Parts Kit for "How a 555 Timer IC Works	\$2.95
MC1-12-PK	Parts Kit for "Burglar Alarm circuit	\$3.95
MC1-13-PK	Parts Kit for "Solar-Activated Night Light circuit	\$3.95
MC1-14-PK	Parts Kit for "0 TO 9V DC Power Supply circuit	\$2.95
MC1-15-PK	Parts Kit for "Electronic Metronome circuit	\$4.95
MC1-16-PK	Parts Kit for "Electronic Motorcycle circuit	\$3.95
MC1-17-PK	Parts Kit for "Railroad Lights circuit	\$2.95
MC1-18-PK	Parts Kit for "Variable Speed Lights circuit	\$3.95
MC1-19-PK	Parts Kit for "Continuity Tester circuit	\$4.95
MC1-20-PK	Parts Kit for "Audio Generator circuit	\$5.95
MC1-21-PK	Parts Kit for "Electronic Police Siren circuit	\$4.95
MC1-22-PK	Parts Kit for "Solar-Activated Wake-Up Alarm circuit	\$3.95
MC1-23-PK	Parts Kit for "Variable Timer circuit	\$3.95
MC1-24-PK	Parts Kit for "Moisture Detector circuit	\$2.95
MC1-25-PK	Parts Kit for "Code Oscillator circuit	\$4.95
MC1-26-PK	Parts Kit for "Audible Water Detector circuit	\$4.95
MC1-27-PK	Parts Kit for "English Police Siren circuit	\$4.95
MC1-28-PK	Parts Kit for "Electronic Canary circuit	\$7.95
MC1-29-PK	Parts Kit for "fantasy Space Machine Gun circuit	\$5.95
MC1-30-PK	Parts Kit for "Ultrasonic Pest Repeller circuit	\$5.95
MC1-SET-PK	<b>Complete Set of All Series 1 Parts Kits (31 total)</b>	<b>\$120.00</b>